


# Design Status Report

## EENG530 Final Project Group 3


Names: Jacob Hulvey, Jack Mullen, Dawit Yerdea
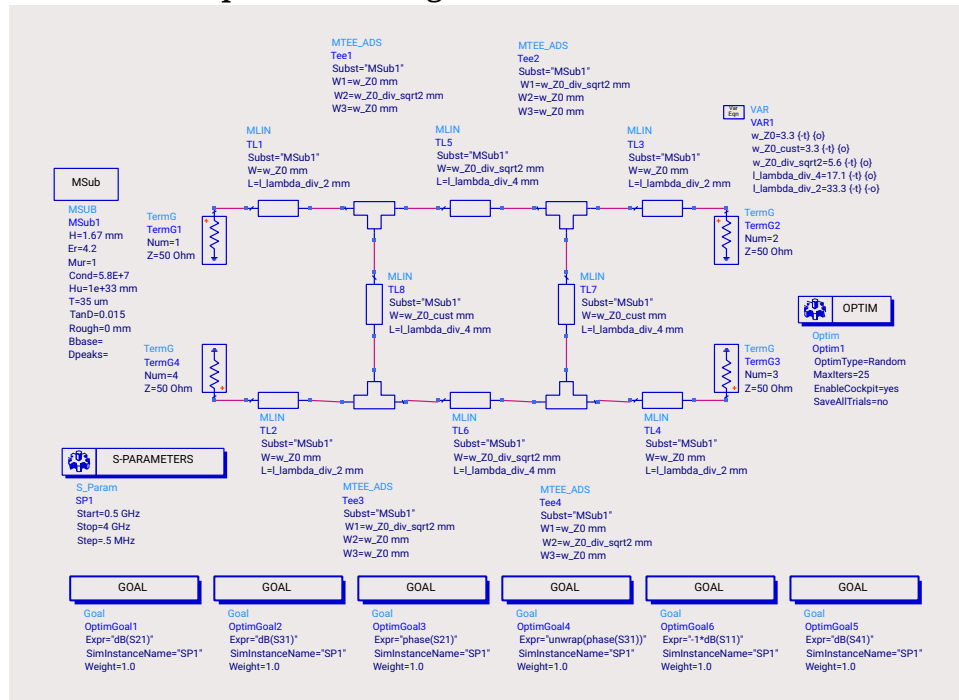
### 90 Degree Branchline Hybrid Coupler:

- We have started tuning/optimizing the implemented microstrip lines but are struggling to meet the required specifications over the full bandwidth.
- Schematic with optimizer and goals:



- Responses with Goals:

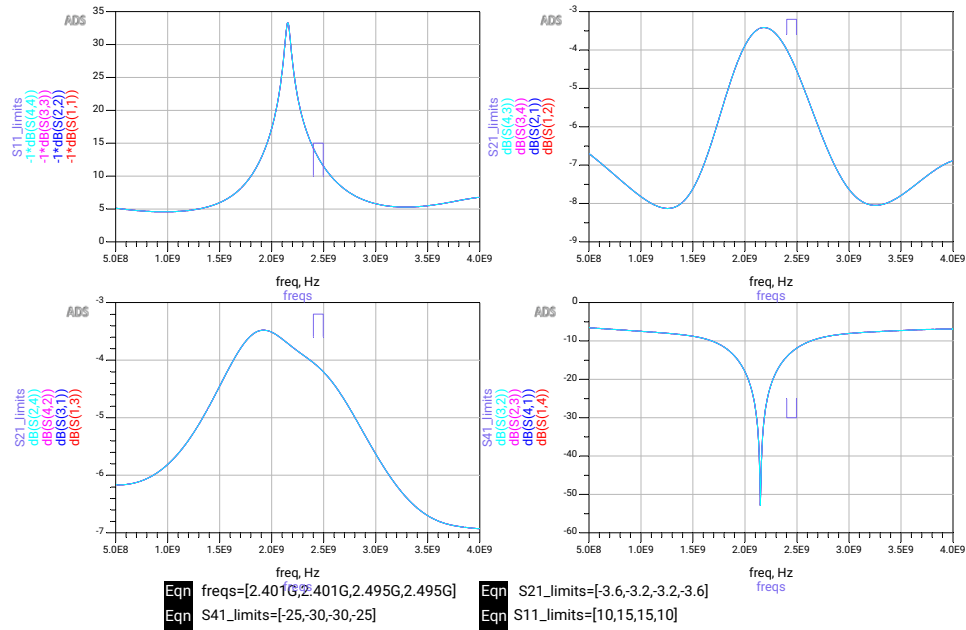

### 90 Degree 20dB coupled-line Coupler:

- We are currently calculating even and odd impedance values and implementing these values within the linecalc tool to achieve the desired effect.
- From here, the plan is to continue tuning dimensional values with the optimization tool to achieve the most ideal effect.
- We are currently a little bit hung up on getting the ideal response from the linecalc output values.

$$\begin{aligned}
 20\text{dB } C &\rightarrow -20\text{dB} = 20 \log |S_{31}| \\
 |S_{31}| &= 0.1 = |C| \\
 |C| &= \frac{Z_0 - Z_c}{Z_0 + Z_c} \rightarrow Z_c = Z_0 \frac{1-C}{1+C} = Z_0 \cdot 0.818182 \\
 Z_c &= \sqrt{Z_0 Z_0} \rightarrow Z_c = \sqrt{\frac{4C}{1-C}} Z_0 = 55.2770798 \\
 Z_0 &= 45.27670179
 \end{aligned}$$

LineCalc/untitled

File Simulation Options Help

Component

Type MCLIN ID MCLIN: CLin1

Substrate Parameters

ID MSub1

H	1.67	mm
Er	4.2	N/A
Mur	1	N/A
Cond	58000000	N/A
Hu	1e+33	mm
T	35	um

Component Parameters

Freq	2.448	GHz
		N/A
		N/A

Physical

W	3.218250	mm
S	2.206810	mm
L	17.174700	mm
		N/A

Synthesize

Analyze

Electrical

ZE	55.277080	Ohm
ZO	45.226702	Ohm
Z0	50	Ohm
C_DB	-20	N/A
E_Eff	90	deg

Calculated Results

KE = 3.43507  
KO = 2.93044  
AE\_DB = 0.105124  
AO\_DB = 0.0920873  
SkinDepth = 0.052585

Values are consistent

LineCalc/untitled

File Simulation Options Help

Component

Type MLIN ID MLIN: TL1

Substrate Parameters

ID MSub1

H	1.67	mm
Er	4.2	N/A
Mur	1	N/A
Cond	58000000	N/A
Hu	1e+33	mm
T	35	um

Component Parameters

Freq	2.448	GHz
Wall1	2.5000000000	mm
Wall2	2.5000000000	mm

Physical

W	3.287130	mm
L	17.096700	mm
		N/A
		N/A

Synthesize

Analyze






Electrical

Z0	50.000000	Ohm
E_Eff	90.000000	deg
		N/A
		N/A

Calculated Results

K\_Eff = 3.20682  
A\_DB = 0.0988891  
SkinDepth = 0.052585

Values are consistent

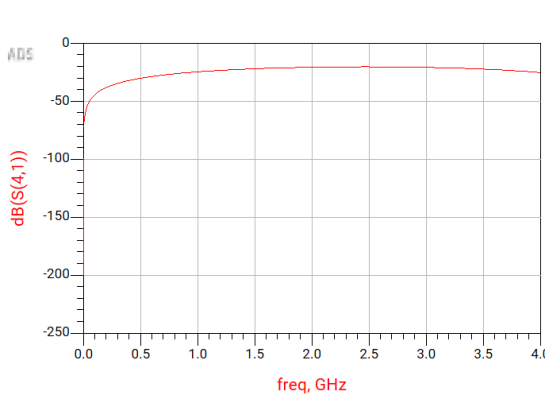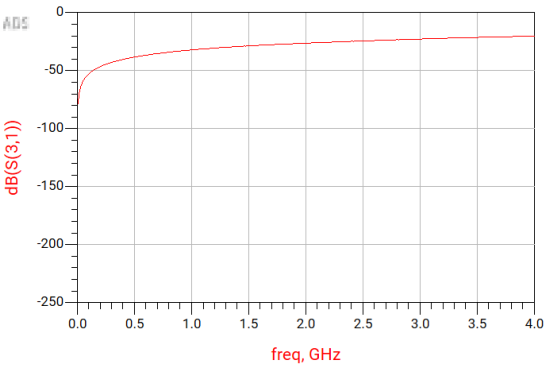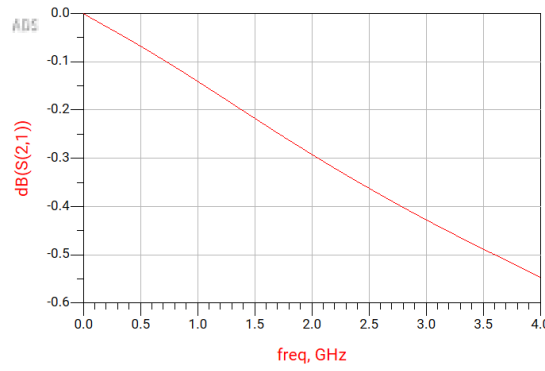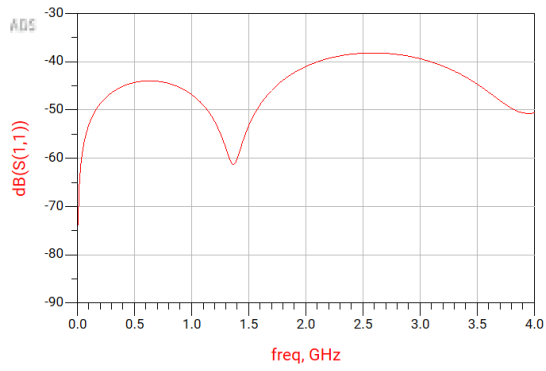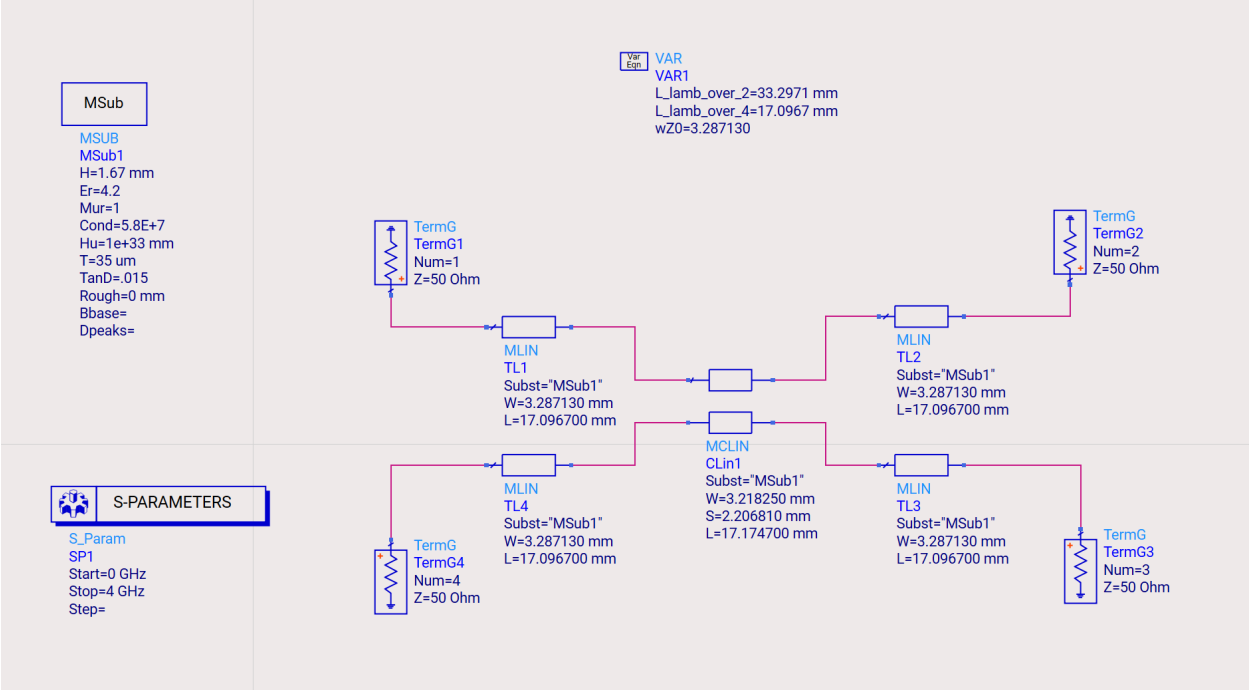

## Chebyshev Bandpass Filter:

- We are currently trying to convert an ideal bandpass filter to a stepped impedance or open stub bandpass filter.
- We have found a Chebyshev table with passband ripple of 0.1 dB (see below). We are going to use this level of passband ripple because the filter will not work as well when we round to 0.1 mm increments due to manufacturing limitation.

$n$	$R_S/R_L$	$C_1$	$L_2$	$C_3$	$L_4$	$C_5$	$L_6$	$C_7$
5	1.000	1.301	1.556	2.241	1.556	1.301		
	0.900	1.285	1.433	2.380	1.488	1.488		
	0.800	1.300	1.282	2.582	1.382	1.738		
	0.700	1.358	1.117	2.868	1.244	2.062		
	0.600	1.470	0.947	3.269	1.085	2.484		
	0.500	1.654	0.778	3.845	0.913	3.065		
	0.400	1.954	0.612	4.720	0.733	3.886		
	0.300	2.477	0.451	6.196	0.550	5.237		
	0.200	3.546	0.295	9.127	0.366	7.889		
	0.100	6.787	0.115	17.957	0.182	15.745		
	$\infty$	1.561	1.807	1.766	1.417	0.651		
6	1.355	0.942	2.080	1.659	2.247	1.534	1.277	
	1.429	0.735	2.249	1.454	2.544	1.405	1.029	
	1.667	0.542	2.600	1.183	3.064	1.185	2.174	
	2.000	0.414	3.068	0.958	3.712	0.979	2.794	
	2.500	0.310	3.765	0.749	4.651	0.778	3.645	
	3.333	0.220	4.927	0.551	6.195	0.580	4.996	
	5.000	0.139	7.250	0.361	9.261	0.384	7.618	
	10.000	0.067	14.220	0.178	18.427	0.190	15.350	
	$\infty$	1.534	1.884	1.831	1.749	1.394	0.638	
7	1.000	1.262	1.520	2.239	1.680	2.239	1.520	1.262
	0.900	1.242	1.395	2.361	1.578	2.397	1.459	1.447
	0.800	1.255	1.245	2.548	1.443	2.624	1.362	1.697
	0.700	1.310	1.083	2.819	1.283	2.942	1.233	2.021
	0.600	1.417	0.917	3.205	1.209	3.384	1.081	2.444
	0.500	1.595	0.753	3.764	0.928	4.015	0.914	3.018
	0.400	1.885	0.593	4.618	0.742	4.970	0.738	3.855
	0.300	2.392	0.437	6.054	0.556	6.569	0.557	5.217
	0.200	3.428	0.286	8.937	0.369	9.770	0.372	7.890
	0.100	6.570	0.141	17.603	0.184	19.376	0.180	15.813
	$\infty$	1.575	1.858	1.921	1.827	1.734	1.379	0.631
$n$	$R_S/R_L$	$L_1$	$C_2$	$L_3$	$C_4$	$L_5$	$C_6$	$L_7$

- Using the 7<sup>th</sup> order filter coefficients above we converted to real lumped element capacitance and inductance:

Original Type	Original L and C Lowpass	Lowpass Type	Highpass	Highpass Type	Bandpass Inducto	Bandpass Capacito	Bandpass Inductor n	Bandpass Capacitor p	Bandpass Type
1 series L	1.262 4.103E-09	series L	1.031E-12	series C	1.06837E-07	3.95782E-14	106.8369884	0.039578189	series L and C
2 shunt C	1.52 1.977E-12	shunt C	2.139E-09	shunt L	8.21508E-11	5.14714E-11	0.08215078	51.47138585	shunt L and C
3 series L	2.239 7.28E-09	series L	5.809E-13	series C	1.89547E-07	2.2308E-14	189.5467647	0.022308028	series L and C
4 shunt C	1.68 2.185E-12	shunt C	1.935E-09	shunt L	7.43269E-11	5.68894E-11	0.074326896	56.88942647	shunt L and C
5 series L	2.239 7.28E-09	series L	5.809E-13	series C	1.89547E-07	2.2308E-14	189.5467647	0.022308028	series L and C
6 shunt C	1.52 1.977E-12	shunt C	2.139E-09	shunt L	8.21508E-11	5.14714E-11	0.08215078	51.47138585	shunt L and C
7 series L	1.262 4.103E-09	series L	1.031E-12	series C	1.06837E-07	3.95782E-14	106.8369884	0.039578189	series L and C
20	50								
N	7								
omega_c	15378402494								
f_c	2447548774								
f_min	2401000000								
f_max	2495000000								
delta	0.038405772								

- 
- TermG1  
TermG1  
Num=1  
Z=50 Ohm
- C1  
C1=0.039578189 pF
- L1  
L1=106.8369884 nH  
R=
- C2  
C2=51.47138585 pF
- L2  
L2=0.08215978 nH  
R=
- C3  
C3=0.022308028 pF
- L3  
L3=0.07432696 nH  
R=
- C4  
C4=56.88942647 pF
- L4  
L4=189.5467647 nH  
R=
- C5  
C5=0.022308028 pF
- L5  
L5=189.5467647 nH  
R=
- C6  
C6=51.47138585 pF
- L6  
L6=0.08215978 nH  
R=
- C7  
C7=0.039578189 pF
- L7  
L7=106.8369884 nH  
R=
- TermG2  
TermG2  
Num=2  
Z=50 Ohm
- S-PARAMETERS**
- S\_Param  
SP1  
Start=0.5 GHz  
Stop=4 GHz  
Step=1 MHz
- | Port1 | Port2 | S11    | S21  | S12    | S22    |
|-------|-------|--------|------|--------|--------|
| 1     | 2     | -40.00 | 0.00 | -40.00 | -40.00 |

- 

- 
- The image shows a schematic diagram of a transmission line model in ADS 2012.04. The model consists of a series of T-junctions and MLOC components. The schematic is divided into sections by MLOC components, with parameters for each section. The model is configured for a 50 Ohm termination and a 50 Ohm load. The schematic is titled 'MSub' and includes a 'S-Parameters' block, an 'OPTIM' block, and a 'GOAL' block. The 'S-Parameters' block is configured for a 50 Ohm load and a 50 Ohm source. The 'OPTIM' block is configured for a 50 Ohm load and a 50 Ohm source. The 'GOAL' block is configured for a 50 Ohm load and a 50 Ohm source.
- MSub**
- MSUB  
MSub1  
H=1.67 mm  
Er=42  
Mur=1  
Cond=5.8E+7  
Hu=1e+33 mm  
T=35 um  
TanD=0.015  
Rough=0 mm  
Bbase=0  
Dpeaks=
- S-Parameters**
- S\_Param  
SP1  
Start=0.5 GHz  
Stop=4 GHz  
Steps: 5 MHz
- OPTIM**
- Optim  
Optim1  
OptimType=Random  
MaxIters=1000  
UseAllOptVars=yes  
EnableCockpit=yes  
SaveAllTrials=no
- GOAL**
- Goal  
OptimGoal1  
Expr=db(S21)  
SimInstanceName="SP1"  
Weight=1
- GOAL**
- Goal  
OptimGoal2  
Expr=-1\*db(S11)  
SimInstanceName="SP1"  
Weight=1
- VAR**
- VAR1  
ldiv2=16.6378 (o)  
w9=0.15823 (o)  
ldiv4=17.1  
w10=5.60664 (o)  
w11=0.294279 (o)  
w2=6.51209 (o)  
w3=0.280237 (o)  
w4=6.56909 (o)  
w5=9.02133 (o)  
w6=5.27506 (o)  
w7=2.98173 (o)
- VAR**
- VAR2  
w1=0.179202 (o)  
w8=8.95808 (o)  
w9=0.15823 (o)  
w10=5.60664 (o)  
w11=0.294279 (o)  
w2=6.51209 (o)  
w3=0.280237 (o)  
w4=6.56909 (o)  
w5=9.02133 (o)  
w6=5.27506 (o)  
w7=2.98173 (o)