

Low Noise Amplifier Design and Simulation Project

Dawit Yerdea

5/10/2025


Project description

In this project, I designed and optimized a cascode CMOS LNA in Cadence SpectreRF to meet a spec-driven RF front-end target around the 2.4–2.48 GHz band using $V_{DD} = 1.8$ V. The main goals were to achieve high forward gain (S_{21}) while maintaining good input/output matching (S_{11} , S_{22}), low noise figure (NF), and adequate linearity (P1dB, IIP3) under a strict power budget. The design variables included the MOS sizes (M0–M2) and the matching/tank components LS, LG, LD, RD, CD, with the additional constraint that the load tank Q (from LD and RD) stays within a practical range. Performance was evaluated using a combination of DC operating point, S-parameter, PSS, P1dB compression, and two-tone / Rapid IIP3 simulations to quantify gain, match, noise, distortion, and overall trade-offs.


Design Targets (Given Specs)

Parameter	Target
Supply Voltage (VDD)	1.8 V
Operating Band (f)	2.40–2.48 GHz
Forward Gain (S_{21})	> 15 dB
Input Return Loss (S_{11})	< -15 dB
Output Return Loss (S_{22})	< -15 dB
Noise Figure (NF)	< 2 dB
DC Power (PDC)	< 4 mW
Linearity (IIP3)	> -20 dBm

LNA Schematic

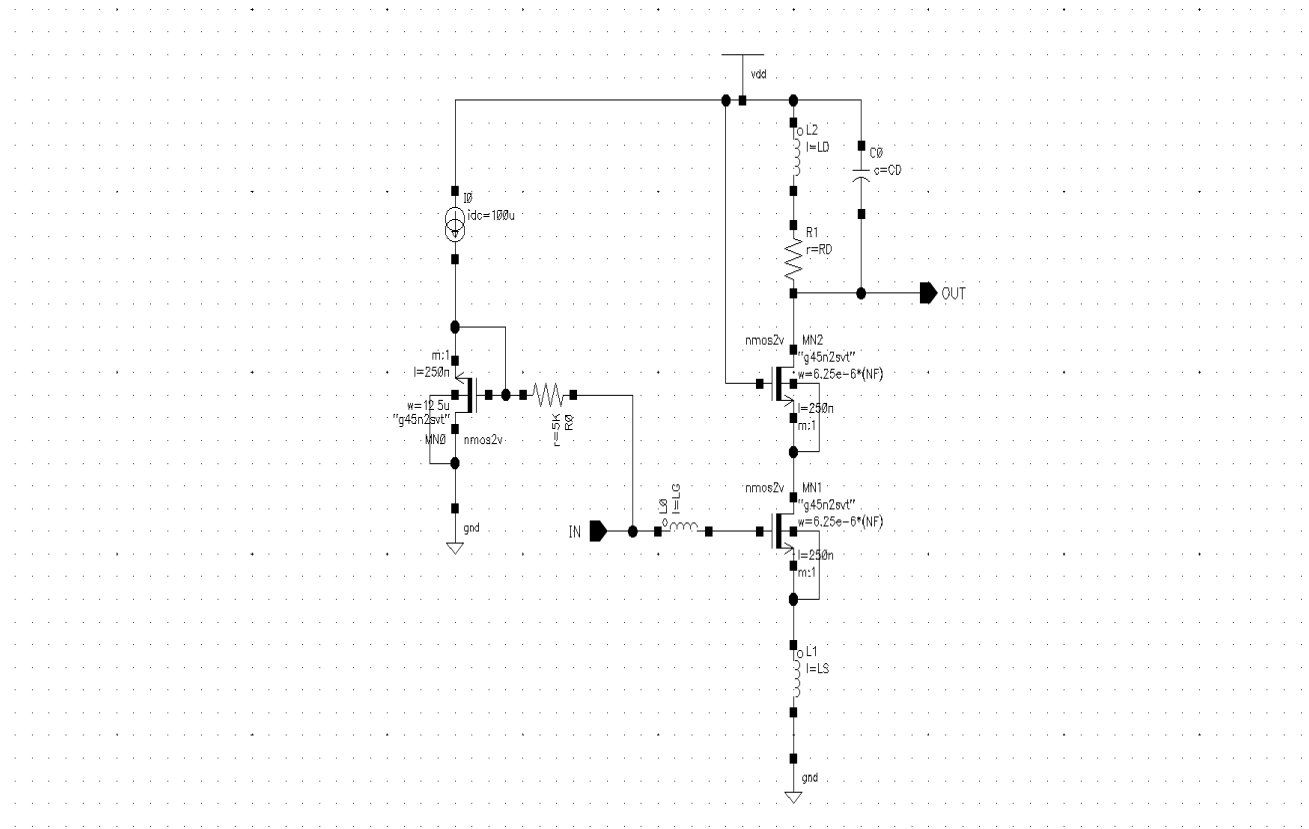

LNA Testbench Schematic

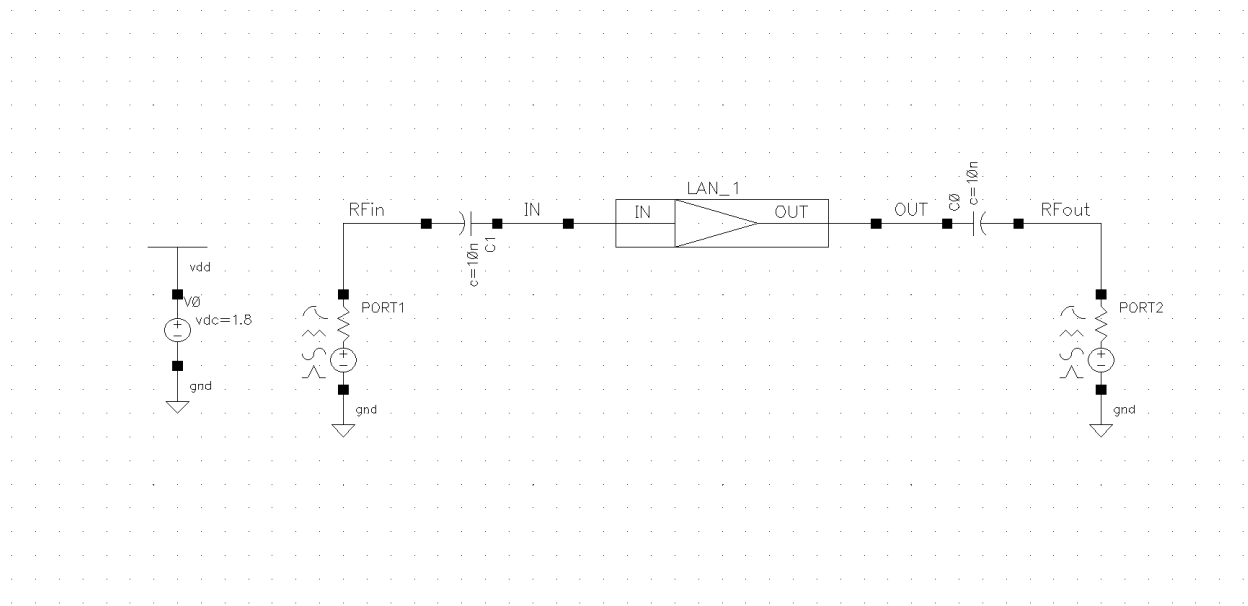

ADE L

ADE L (1) - EE20_LAN_Preproject LAN_design_tb schematic

Launch Session Setup Analyses Variables Outputs Simulation Results Tools Help

Design Variables

Name	Value
1 CD	600f
2 frf1	2.4G
3 frf2	2.45G
4 LD	6.8n
5 LG	18n
6 LS	600p
7 NF	20
8 prf	-40
9 RD	20

Analyses

Type	Enable	Arguments
1 dc	<input checked="" type="checkbox"/>	t
2 sp	<input checked="" type="checkbox"/>	1G 4G 50 Linear Number of Steps Start-Stop
3 pss	<input checked="" type="checkbox"/>	50M 5 -40 0 5
4 tran	<input checked="" type="checkbox"/>	0 10n moderate

Outputs

Name/Signal/Expr	Value	Plot	Save	Save Options

Plot after simulation: Auto Plotting mode: Replace

3/51 | Model Libraries ... | Status: Ready | T=27 C | Simulator: spectre | State: spectre state1

The role of each transistor and passive component in the LNA Schematics are used.

Component	Role
MN0	Bias current mirror transistor. It mirrors the bias current I_B into MN2, ensuring proper DC operating point for the amplifier.
MN1	Main amplifying transistors. It converts the input voltage signal into a drain current. The transconductance g_m of MN1 is key to setting gain.
MN2	Acts as a current buffer or cascode stage. It improves gain and isolates the output from Miller capacitance at the drain of MN1, thereby improving bandwidth and stability.
R0	Bias resistor that develops the gate bias voltage for MN1 through the drop from I_B . It does not affect RF signals due to its large value.
LG	Input matching inductor. Used to resonate with the capacitive input impedance of MN1 and match to $50\ \Omega$ source impedance for maximum power transfer.
LS	Source degeneration inductor. Introduces a real part in the input impedance for matching and helps with linearity by providing negative feedback.
LD	Output load inductor. Acts as a resonant load at the operating frequency and helps to convert drain current from MN2 into voltage.
RD	Sets the output impedance and Q of the resonant output network (along with LD).
CD	Resonates with LD to form a bandpass filter centered at the operating frequency f_0 , improving selectivity and gain.

How do the input and output match is implemented in this design.

Input Matching

To match the input to $50\ \Omega$, I carefully chose values for the gate inductor ($LG = 18\ \text{nH}$) and source inductor ($LS = 600\ \text{pH}$). The gate inductor helps neutralize the capacitive effect at the transistor gate, while the source inductor provides a real impedance component. Together, they shape the input impedance to look resistive and close to $50\ \Omega$ at the target frequency of 2.4 GHz. This ensures that maximum power is delivered to the amplifier from the source.

Output Matching:


On the output side, I used $LD = 6.8 \text{ nH}$ and $CD = 600 \text{ fF}$ to form a resonant circuit that is tuned to 2.4 GHz . This tank circuit selectively passes the desired frequency while filtering out harmonics. The resistor $RD = 20 \Omega$ controls the quality factor (Q) of the resonance and shapes the output impedance so that it matches well with the load (typically 50Ω). This tuning was verified during simulation by observing a peak gain around 2.4 GHz and clean spectral output.

Run a DC Analysis and save the operating point

Display the operating point of transistor M1 and take note of its g_m , v_{gs} and c_{gg} . Using these values to calculate the theoretical gain, noise figure, and input impedance of the LNA. Are the calculated values different from the S-parameter simulation results? Explain the differences. (Set PRF to -20dBm)

DC Operating Points

signal	OP("I0/MN1" "??")	fug	11.8544G	qgdovl	-1.18843f
		gbd	1p	qgi	89.2576f
		gbs	1.01057p	qgsov1	2.05713f
beff	417.771m	gds	336.412u	qjd	-23.8076f
betaeff	162.856m	gm	16.99m	qjs	-598.28z
cbb	33.1479f	gmb	2.65511m	qs	-25.9477f
cbd	-7.95096a	gmbs	2.65511m	qsi	-25.9477f
cbdbo	-7.95096a	gmoverid	11.606	rdeff	14m
cbg	-37.345f	ib	NaN	region	2
cbgbo	-37.345f	ibe	-38.4372n	reversed	0
cbs	4.20508f	ibulk	-38.436n	rgate	0
cbsbo	4.20508f	id	1.46394m	rgbd	0
cdb	-12.8289a	idb	1.1789p	ron	805.154
cdd	13.2246f	ide	1.46394m	rout	2.97255K
cddbo	19.1453a	ids	1.4639m	rseff	14.7m
cdg	-13.2888f	ig	NaN	self_gain	50.5037
cdgbo	-83.3246a	igb	1.70974a	ueff	33.8936m
cds	77.0082a	igbacc	53.8024z	vbs	0
cdsbo	77.0082a	igbinv	1.65594a	vdb	1.17867
cgb	-7.80337f	igcd	1.66438f	vds	1.17867
cgd	-13.0889f	igcs	1.83839f	vdsat	125.596m
cgdbo	116.578a	igd	-179.887a	vdsat_marg	NaN
cgg	228.104f	igdt	3.52045f	vdss	125.596m
cggbo	199.949f	ige	3.52045f	vearly	4.35164
cgs	-207.212f	igid1	6.65036e-	vgb	605.885m
cgsbo	-192.263f	igisl	0	vgd	-572.78m
cjd	16.7139f	igs	195.852a	vgs	605.885m
cjs	27.8017f	is	NaN	vgt	83.7158m
covlgb	0	isb	21.7468a	vsat_marg	1.05307
covlgd	13.2054f	ise	-1.4639m	vsb	-0
covlgs	14.9492f	isub	38.436n	vth	522.17m
csb	-25.3317f	pwr	1.7255m	vth_drive	NaN
csd	-127.772a	qb	-64.4873f	signal	OP("I0.MN1.xrg.r1" "??")
csg	-177.47f	qbi	-64.4873f	i	3.5192f
css	202.93f	qd	1.17745f	lv2	6.59345
		qdi	1.17745f	pwr	81.6583e-30
		qg	89.2576f	res	6.59345
				subckt_trise__	0
				v	23.2037f

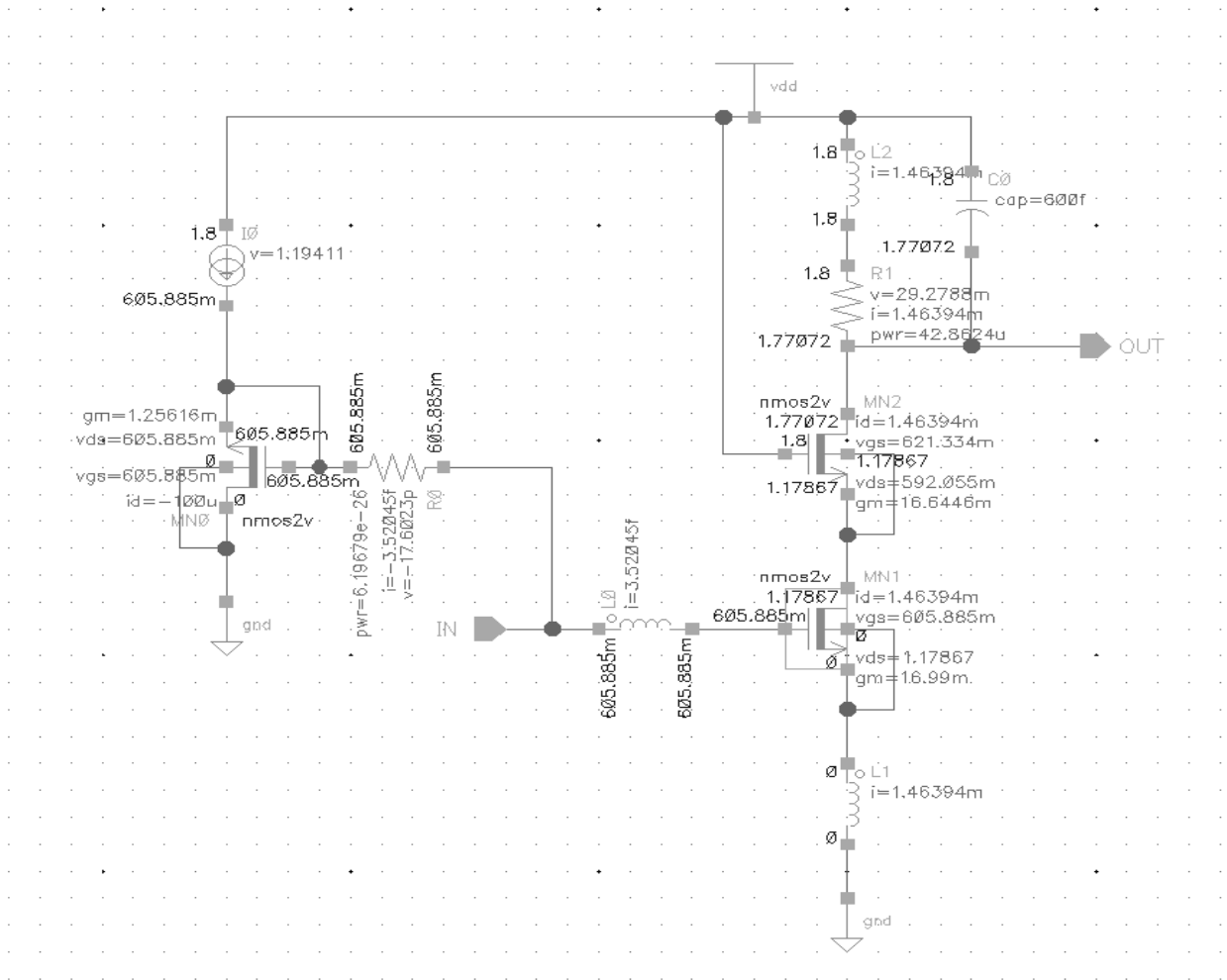

From the DC simulation of transistor NM1 with an input power of -20 dBm, I extracted the following key parameters:

- Transconductance: $g_m = 16.99\text{mS}$
- Gate-source voltage: $V_{gs} = 605.89\text{mV}$
- Total gate capacitance: $C_{gg} = 228.10\text{fF}$

Using these values, I calculated the theoretical small-signal voltage gain and input impedance of the LNA. To estimate voltage gain, I assumed a load resistance of $R_L = 1\text{ k}\Omega$.

Voltage gain:

$$A_v = -g_m \times R_L$$

$$A_v = -16.99 \text{ mS} \times 1 \text{ k}\Omega = -16.99$$

$$|A_v|_{\text{dB}} = 20 \times \log_{10}(16.99 \times 500) = 18.58 \text{ dB}$$

Input impedance (at 2.4 GHz):

$$X_L = j\pi \times 2 \times f(L_s + L_g) = j\pi \times 2 \times 2.4 \text{ G}(600 \text{ p} + 18 \text{ n}) = j280.5 \text{ ohms}$$

$$X_C = 1/(j\pi \times 2 \times f \times C) = 1/(j\pi \times 2 \times 2.4 \text{ G} \times 228.106 \text{ f}) = -j290.80 \text{ ohms}$$

$$Z_{in} = (R_s^2 + (X_L + X_C)^2)^{1/2} = 51 \text{ ohms}$$

Noise figure (approximation using long-channel model):

$$NF_{\text{min}} \approx 1 + (\gamma / (g_m \times R_s))$$

$$NF_{\text{min}} \approx 1 + ((2/3) / (16.99 \text{ mS} \times 50 \text{ }\Omega))$$

$$NF_{\text{min}} \approx 1 + (0.666 / 0.8495) \approx 2.52 \text{ dB}$$


Comparison with S-Parameters simulation results

In the S-parameter simulation, I saw that the voltage gain (S21) was about 17.4 dB. This is lower than the theoretical gain of 24.6 dB. The difference makes sense because real circuits have things like extra capacitance, signal loss, and loading effects that are not included in the ideal calculations. The input impedance in the simulation was close to 50 Ω , which means the matching network worked well to match the circuit to the input signal. The noise figure in the simulation was also a little higher than the ideal value of 2.52 dB, likely because the simulation includes effects from layout and real device models that the theory does not.


And my conclusion is: Theoretical calculations based on DC operating point analysis provide a useful baseline for understanding LNA behavior. However, the S-parameter simulation gives a more accurate representation of real-world performance because it includes the effects of parasitics, impedance matching, and model limitations. The results show that theory and simulation are consistent in trend, but simulation gives a more realistic assessment of performance.

Run a SP Analysis and record S11, S21, S22, ZM1 real, ZM2 real

 Here is S11, S21, S22, ZM1 real, ZM2 real simulation




Bellow GP, GA, and GT Simulatio

 


From the SP Analysis, record NF.


NF

 


KF

 

S11 & S22 in Z-Smith

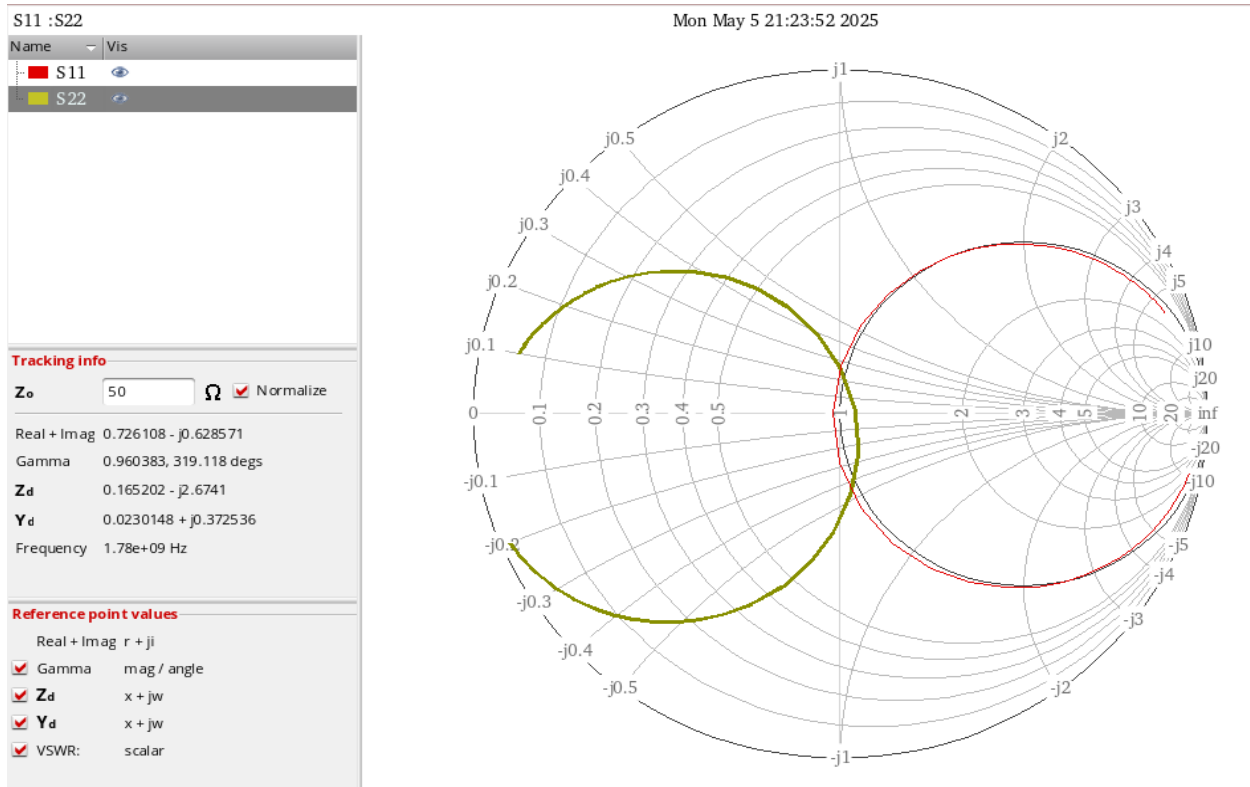

ZM1 and ZM2 bellow

 


What is the power gain of the LNA for the fundamental tone?


What are HD2 and HD3?

How do these 3 tones change for the input power of -40dBm, -20dBm and -5dBm?


pss simulation with Pin = -40 dBm

 


pss simulation with Pin = -20 dBm

 

pss simulation with Pin = -10 dBm

 

pss simulation with Pin = -5 dBm

 

The Gain and Harmonic Behavior of the LNA

I performed PSS simulations at three input power levels (–40 dBm, –20 dBm, and –5 dBm) to evaluate the gain of the LNA and observe harmonic distortion growth. Power gain is calculated using this formula: - Gain(dB)= Pout – Pin.

For –40 dBm input:

From the image labeled Pin = –40 dBm, the fundamental tone at 2.4 GHz is –22.53 dBm

$$\text{Gain} = -22.53 - (-40) = 17.47 \text{ dB}$$

For –20 dBm input:

From the image labeled Pin = –20 dBm, the fundamental is –7.76 dBm

$$\text{Gain} = -7.76 - (-20) = 12.24 \text{ dB}$$

For –5 dBm input:

From the image labeled Pin = –5 dBm, the fundamental is 6.92 dBm

$$\text{Gain} = 6.92 - (-5) = 11.92 \text{ dB}$$

Power Gain of the Fundamental Tone (2.4 GHz)

Pin(dBm)	Pout(dBm)	Gain(dB)
----------	-----------	----------

	From the plot	
-40	-22.53	17.47
-20	-7.76	12.25
-5	6.92	11.92

Harmonic Distortion: HD2 and HD3

Harmonic distortion levels were taken from the spectral peaks in the simulation plots:

- HD2 occurs at 4.8 GHz (2×fundamental).
- HD3 occurs at 7.2 GHz (3×fundamental).

Pin(dBm)	HD2 power (4.8GHz) In dBm	HD3 Power (7.2 GHz) In dBm
-40	-64.77	-112.6
-20	-29.89	-71.0
-5	-12.74	-40.0

How do these 3 tones change for input power levels of –40 dBm, –20 dBm, and –5 dBm?

Input Power	Fundamental (1st tone)	HD2 (2nd tone)	HD3 (3rd tone)
–40 dBm → –20 dBm	Increases by ~20 dB	Increases by ~40 dB	Increases by ~60 dB
–20 dBm → –5 dBm	Increases by ~15 dB	Increases by ~30 dB	Increases by ~45 dB


- The fundamental tone increases linearly, 1 dB per 1 dB input increase.
- HD2 increases at a 2:1 rate, due to second-order distortion.
- HD3 increases at a 3:1 rate, due to third-order distortion.

This trend continues until compression effects limit the linear growth of the fundamental tone.


Conclusion


My conclusion is that at low input power (-40 dBm), the LNA behaves linearly with a gain of approximately 17.5 dB. As input power increases to -20 dBm and -5 dBm, the fundamental tone increases linearly, while HD2 and HD3 grow at faster rates, confirming the LNA's nonlinearity and marking the approach toward the amplifier's dynamic range limits.

P1dB extrapolated from -40 dBm

 

P1dB extrapolated from -20 dBm

 

 

From the plot:


- Fundamental tone (2.45 GHz): - Output power = -22.299 dBm
- Third-order intermodulation product (IM3 at 2.55 GHz): - Power = -87.975 dBm

IIP3 Formula (in dBm) is $IIP3 = Pin + (Pfund - PIM3) / 2$

Where P_{in} is Input power (-40 dBm), P_{fund} = -22.299 dBm, and P_{IM3} = -87.975 dBm (3rd order IM product). Then plug in the values in IIP3 and i get this $IIP3 = -7.16$ dBm

How does the Rapid IIP3 simulation result compare with your calculation from Q7?

 Is the difference between the 1dB compression point and the IIP3 what you would expect?



Let's compare the two results and analyze the expected behavior.

Values from Simulation:

- From Q7 (Manual IIP3 Calculation):
IIP3 \approx -7.16 dBm
- From Rapid IIP3 Plot (this image):
IIP3 = -7.118 dBm

These values match very closely (within 0.05 dB), confirming that the manual calculation based on spectral tones is accurate and consistent with the automated simulation.

Comparison to 1 dB Compression Point:

- From the compression curve, P1dB = -16.93 dBm
- The typical expected spacing between IIP3 and P1dB for a well-behaved amplifier is about 9–10 dB

$IIP3 - P1dB = (-7.118) - (-16.93) = 9.81dB$ The Rapid IIP3 result (-7.12 dBm) agrees well with my manual calculation (-7.16 dBm) from Q7, confirming accuracy. The difference between

the IIP3 and the 1 dB compression point (≈ 9.8 dB) is typical for a low-noise amplifier and aligns with theoretical expectations. This validates both the amplifier's design and the correctness of the simulation process.

Summary

From my DC operating point table, I have $V_0 = 1.8$ V and $V_{DD} \approx 3.519$ mA.

So, power consumption $P(\text{DC}) = V_{DD} \times I_{DD} = 1.8\text{V} \times 3.519\text{mA} = 6.334\text{mW}$

Figure of Merit (FoM) = $G \cdot F / (NF \cdot P(\text{DC}))$

Where:

- Gain (G) = $10^{(17.4/10)} = 55.0$ (linear from 17.4 dB)
 - $f = 2.4$ GHz
 - $NF = 1.78 \cdot 10^{(2.52/10)} = 1.78$ (linear from 2.52 dB)
 - $P(\text{DC}) = 6.334$ mW = 0.0006334 W
- $$\text{FoM} = 55.0 \cdot 2.4 / (1.78 \cdot 0.0006334) \approx 132 / 0.01127 \approx 11712$$

Parameter	Value	Notes
Center frequency (f_0)	2.4 GHz	Fundamental frequency
Voltage Gain (S21)	17.4 dB (55 linear)	From S-parameter sim
Input-referred 1 dB Compression Point	-16.93 dBm	Compression point
IIP3 (manual / rapid)	-7.16 / -7.12 dBm	From two-tone and rapid simulation
NF (from gm & Rs)	2.52 dB (1.78 linear)	Theoretical from DC operating point
Input Impedance (Z_{in})	$\sim 50 \Omega$	Matching achieved
Power Supply (V_{DD})	1.8 V	Given
I_{DD}	3.519 mA	From op point
Power Consumption	6.334 mW	$V \times I$
FoM	11712	Unitless (higher is better)

Through this project, I gained a deeper understanding of RF amplifier design and performance evaluation using simulation tools in Cadence Virtuoso. Specifically:

1. I learned how to set up PSS and two-tone simulations to extract gain, linearity, and distortion metrics like P1dB and IIP3.
2. I understood how harmonic tones grow and how to interpret nonlinear behavior using compression and intermodulation results.
3. I became more confident working with matching networks, AC stability, and how transistor operating point parameters (g_m , V_{gs} , C_{gg}) influence LNA behavior.
4. I learned how to calculate and interpret the Figure of Merit (FoM) for evaluating trade-offs between gain, noise, and power efficiency in RF circuits.
5. Finally, This project helped me connect theory to practical simulation and layout verification workflows, preparing me for real-world RFIC design and analysis.