

Implementation of equation 3

Effective transconductance analysis

LAN topology overview

To the write, their is the LNA Topology and It has three cascode stages.

Stage A; Input LNA stage,


- M1 + Ls,Lg: provides main transconductance & input matching
- Cascode M2 : boosts output resistance & improve isolation
- Tank Load: extends BW and flattens gain

Stage B; Gain boost stage (M3-M6)

- Additional cascode pairs
- Each gain stage is tuned to a slightly different resonant freq & together produced a flat gain

Stage C; Output buffer for impedance matching(M7-M8)

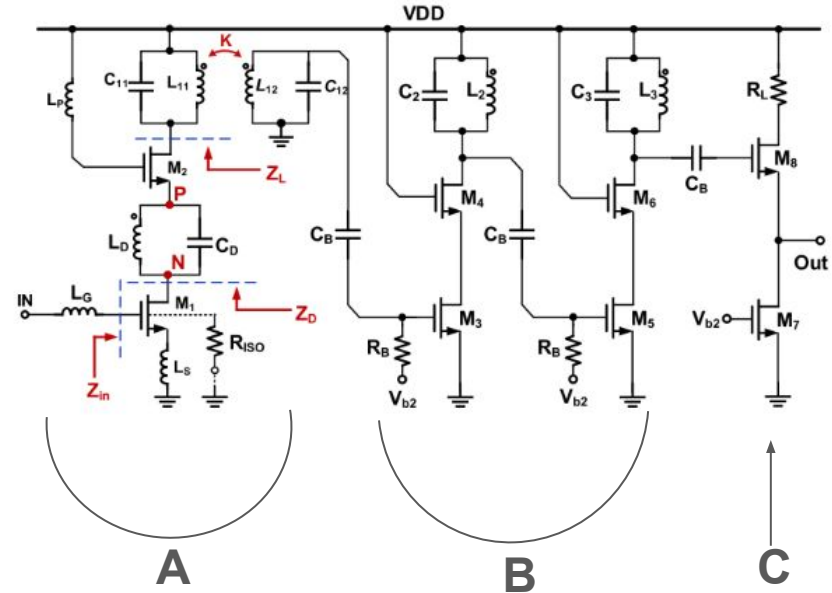- Provides ~ 50 Ohm output matching without adding significant noise.



Derivation of Eqn.(3)

- To the right is the small signal model to derive equation 3.
- Working in the phasor domain ($j\omega$) with voltages V_g , V_x , and V_y .

$$V_{gs1} = V_g - V_s$$

$$\text{Final goal, } G_m = \frac{i_{\text{out}}}{v_{\text{in}}},$$

KCL @ G:

$$\frac{v_g - v_{\text{in}}}{R_S + j\omega L_G} + j\omega C_{gs1}(v_g - v_s) = 0$$

$$\begin{aligned} v_{\text{in}} &= v_g + (R_S + j\omega L_G) j\omega C_{gs1} (v_g - v_s) \\ &= v_g + (R_S + j\omega L_G) j\omega C_{gs1} v_{gs1}. \end{aligned}$$

KCL @ y:

$$\frac{v_s}{j\omega L_S} + j\omega C_{gs1}(v_s - v_g) - g_{m1}v_{gs1} = 0$$


$$v_s = j\omega L_S(j\omega C_{gs1} + g_{m1}) v_{gs1}$$

$$v_g = v_s + v_{gs1} = \left[1 + j\omega L_S(j\omega C_{gs1} + g_{m1})\right] v_{gs1}$$

KCL @ x:

$$g_{m1}v_{gs1} = (j\omega C_{gs2} + g_{m2}) v_x$$
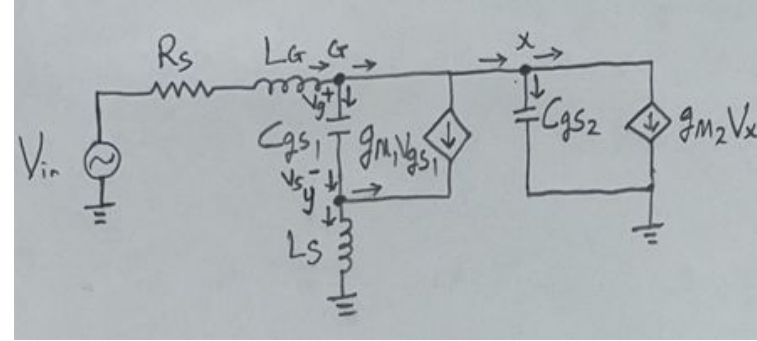
$$v_x = \frac{g_{m1}}{j\omega C_{gs2} + g_{m2}} v_{gs1}, \quad i_{\text{out}} = g_{m2}v_x = \frac{g_{m1}g_{m2}}{j\omega C_{gs2} + g_{m2}} v_{gs1}$$



Setups

- R_s = source impedance 50 ohm
- Output is grounded
- To characterized only transistor stack, load replaced with an AC short to ground (Removed LD, CD, LP)

Derivation of Eqn.(3) continued ...

Relate V_{gs1} to V_{in}

$$\begin{aligned} v_{in} &= \left[1 + j\omega L_S(j\omega C_{gs1} + g_{m1}) \right] v_{gs1} + (R_S + j\omega L_G) j\omega C_{gs1} v_{gs1} \\ &= \left[1 + j\omega(g_{m1}L_S + C_{gs1}R_S) - \omega^2 C_{gs1}(L_S + L_G) \right] v_{gs1}. \end{aligned}$$

Hence,
$$\frac{v_{gs1}}{v_{in}} = \frac{1}{1 + j\omega(g_{m1}L_S + C_{gs1}R_S) - \omega^2 C_{gs1}(L_S + L_G)}$$

Regroup the M1 denominator as $j\omega [C_{gs1}(R_S + j\omega(L_S + L_G)) + g_{m1}L_S]$

Then, the full expression becomes;

$$G_m(j\omega) = \frac{g_{m2}}{j\omega C_{gs2} + g_{m2}} \cdot \frac{g_{m1}}{j\omega C_{gs1}(R_S + j\omega(L_S + L_G)) + j\omega g_{m1}L_S}$$

Poles and Zeros

Transconductance:
$$G_m(j\omega) = \underbrace{\frac{g_{m2}}{j\omega C_{gs2} + g_{m2}}}_{\text{cascode factor}} \cdot \underbrace{\frac{g_{m1}}{j\omega C_{gs1}(R_S + j\omega(L_S + L_G)) + j\omega g_{m1}L_S}}_{\text{M1+input network}}$$

Two Poles: root of $A(j\omega)^2 + B(j\omega) + 1 = 0$

Numerical values ; $g_{m1} = 0.22 \text{ S}$, $g_{m2} = 0.10 \text{ S}$,
 $C_{gs1} = 0.24 \text{ pF}$, $C_{gs2} = 0.24 \text{ pF}$ (assumed),
 $L_S = 0.25 \text{ nH}$, $L_G = 0.85 \text{ nH}$, $R_S = 50 \Omega$.

M1 + input network

Compute the coefficient : - $A = C_{gs1}(L_S + L_G) = 0.24 \text{ pF} \cdot (1.10 \text{ nH}) = 2.64 \times 10^{-22}$

$$B = g_{m1}L_S + C_{gs1}R_S = (0.22)(0.25 \text{ nH}) + (0.24 \text{ pF})(50) = 6.7 \times 10^{-11}$$

Quadratic poles (convert to HZ with $f = \omega/2\pi$) ;

$$f_{p1} \approx \frac{1}{2\pi} \cdot \frac{B - \sqrt{B^2 - 4A}}{2A} = 2.53 \text{ GHz}$$
$$f_{p2} \approx \frac{1}{2\pi} \cdot \frac{B + \sqrt{B^2 - 4A}}{2A} = 37.86 \text{ GHz}$$

Poles and Zeros continued ...

Cascode Pole: $f_{p,CG} = \frac{1}{2\pi} \cdot \frac{g_{m2}}{C_{gs2}} = \frac{0.10}{2\pi \cdot 0.24 \text{ pF}} = 66.31 \text{ GHz}$

No Zeros: Since, both the numerators are constant, g_{m1} and g_{m2} .

Effective Transconductance

$$G_{m1} = \left(\frac{g_{m1}}{j\omega C_{gs1}(j\omega L_S + j\omega L_G + R_S) + j\omega g_{m1} L_S} \right) \cdot \left(\frac{g_{m2}}{j\omega C_{gs2} + g_{m2}} \right)$$

- Shows how Gm1 decreases as frq. Increases due to reactive term- Cgs1,LS,LG , and Cgs2
- **Cgs2** :- assumed ≈ 0.24 pF(Size matched to M1) , sensitivity sweep confirms only high frequency roll-off shifts
- **Gm1** is complex : - has magnitude (gain) and phase

Cascode Factor Equation

$$\underbrace{\frac{g_{m2}}{j\omega C_{gs2} + g_{m2}}}_{\text{cascode factor}}$$

The Low-frequency vs High-frequency behaviour

- At low freq :- $j\omega C_{gs2} \ll g_{m2}$, cascode Factor ≈ 1
- At high freq :- $j\omega C_{gs2} \gg g_{m2}$, cascode factor $\sim 1/(j\omega C_{gs2})$ so it drops off
- The corner Condition -3 dB point when :-

$$\omega C_{gs2} = g_{m2} \longrightarrow f_c = \frac{g_{m2}}{2\pi C_{gs2}} = \frac{0.10}{1.5079644 \times 10^{-12}} \approx 6.63 \times 10^{10} \text{ Hz} \approx 66.3 \text{ GHz}.$$

Take the magnitude of the Cascode Factor and substitute $g_{m2} = 0.10 \text{ S}$,
 $C_{gs2} = 0.24 \text{ pF}$

$$\longrightarrow \frac{g_{m2}}{\sqrt{g_{m2}^2 + g_{m2}^2}} = \frac{1}{\sqrt{2}} \approx 0.707 \text{ } (-3.01 \text{ dB}).$$

- Magnitude drops to 0.707 (-3 dB) at f_c


$|G_{m1}|$ vs Freq. plot

Why $|G_m|$

- because the complex G_m itself hard to visualize
- Magnitude shows the strength of the transistor vs freq.
- $|G_{m1}|$ tells me how much output current i get from a small input voltage and the load then converts that current into voltage and that what's i finally measure as an amplifier gain.

Plot shows

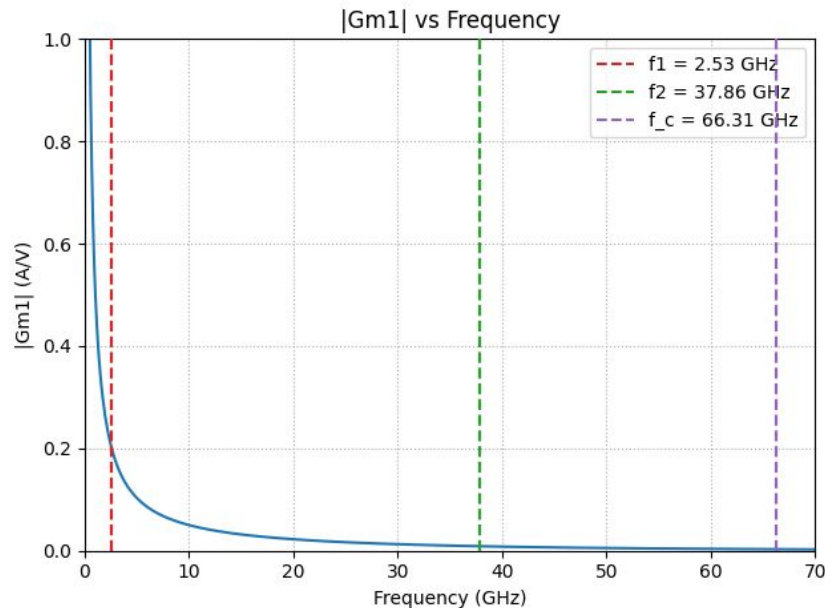- The first stage alone can not keep G_{m1} flat at high freq., parasitic caps & inductors limits it
- The paper added transformer tank load with dual resonance to compensate for this natural roll-off & flatten the over all gain
- Larger C_{gs2} can cause earlier roll-off
- Shows that M1 + M2 pair loses strength as freq increases.




Phase of Gm1 vs Frequency Plot

Why Look at Phase

- Shows the relationship b/n input V and output current
- Shows timing delay between V_{in} and output current
- Important for stability, group delay, and overall amplifier behaviour when cascading stage

Plot shows

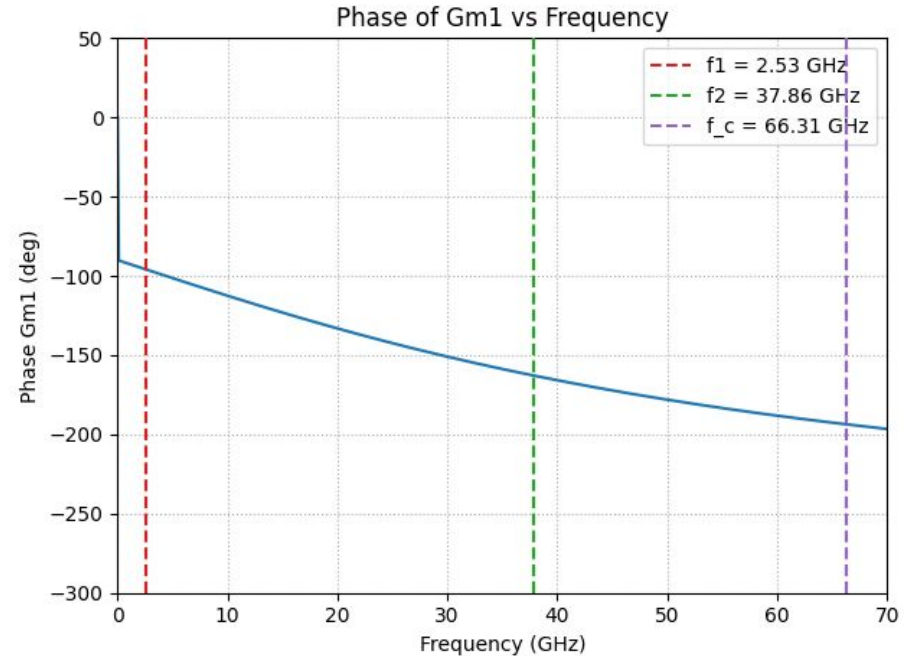- At f_1 : phase $\approx -98^\circ$ (output current is lagging the input voltage by about 98°) almost quadrature
- At f_2 : Phase $\approx -153^\circ$ more lag
- At f_c : Phase $\approx -189^\circ$
- Trend : smooth but lag increases with frequency
- Its stable no sharp jump




Sensitivity Sweep Cgs2 Plots

Why Cgs2 is important

- It sets high-frequency pole(corner frq.) of the cascode device, beyond gain cant stay flat anymore
- Large Cgs2 - lower pole frequency- earlier gain roll-off
- Small Cgs2 - higher pole frequency - wider bandwidth
- Controlled by the size of M2

Plot shows

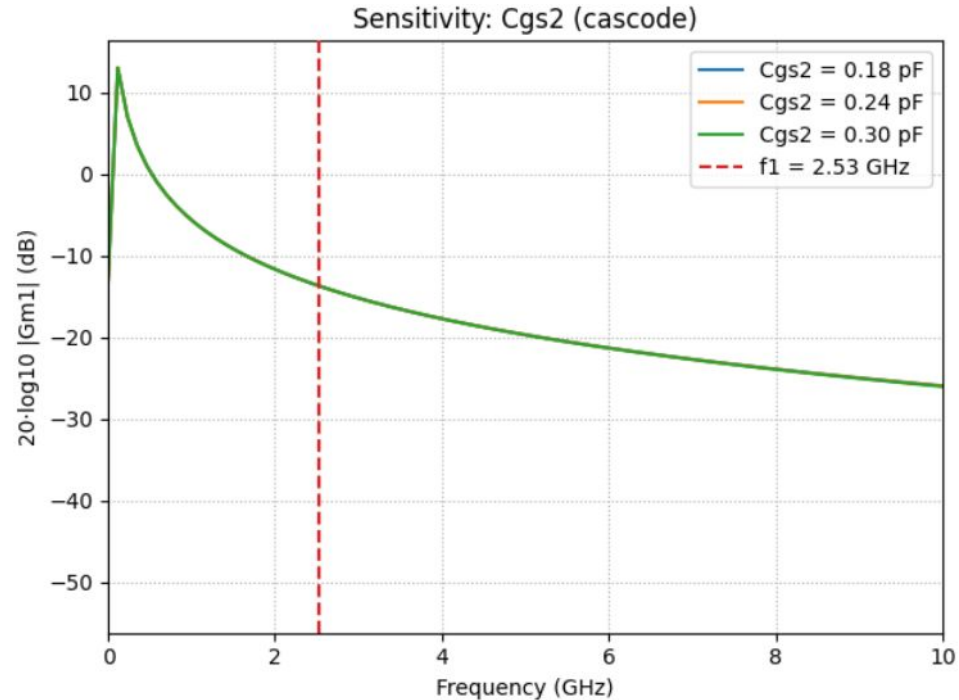- Cgs2 = 0.18,0.24,0.30 pF curves are overlapped
- Zoomed plot, to show the behaviour in lower freq.




Sensitivity Sweep Cgs2 with High frequency Plots

Plot shows

- $C_{gs2} = 0.18, 0.24, 0.30$ pF curves are separated with high frequency
- For the band 4 - 8 GHz, the corner frq. is way up even with $C_{gs2} = 0.24$ pF so the roll-off won't hurt the band

Trade-offs

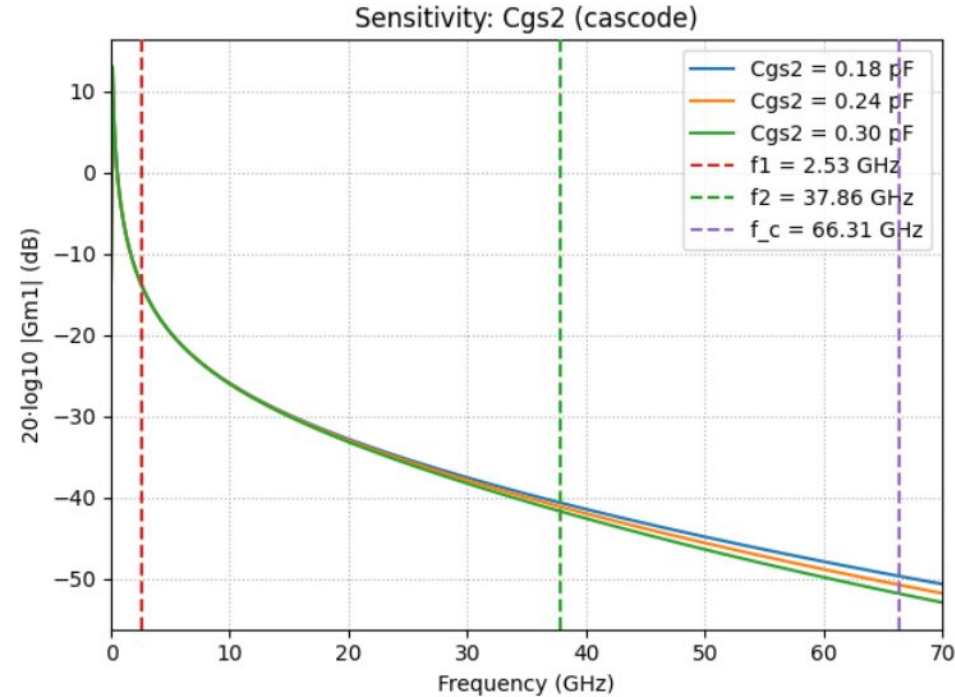
- Large M_2 - unnecessary capacitance hurts BW
- Small M_2 - poor isolation from M_1 's drain leads to worse NF
- Recommendation:- the good spot is choosing M_2 just big enough to give good cascode isolation while keeping C_{gs2} modest so the pole/corner frq stays far above the design BW



The effect of high frequency pole

Plot shows


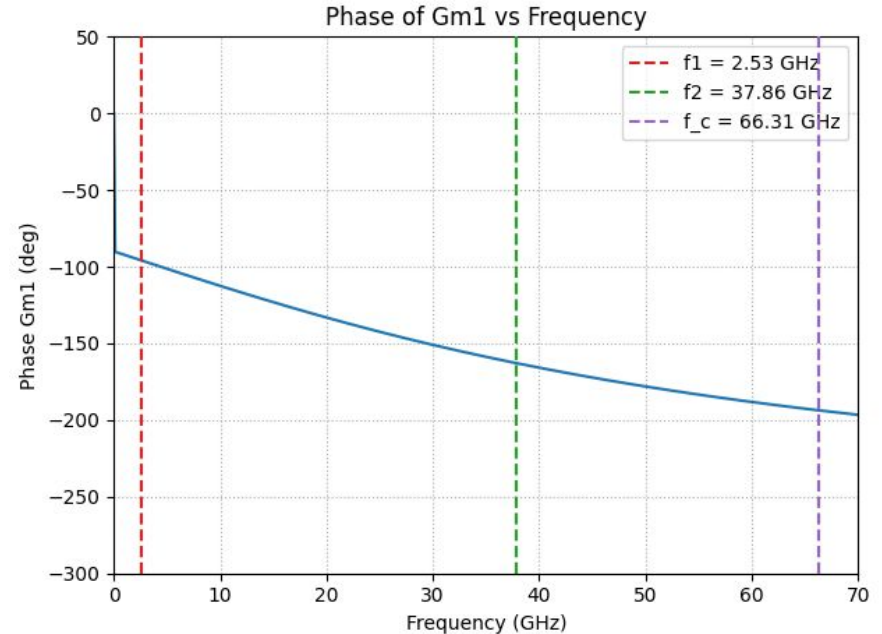
- Higher freq. the cascode device can't keep up
- Shows -90 degree shift
- Shows the output current lags (comes later) & shrinks as freq. increases
- Below the Band of interest 4 - 8 GHz, the cascode passes the signal almost normal



Sensitivity to Ls Sweep

Plot shows

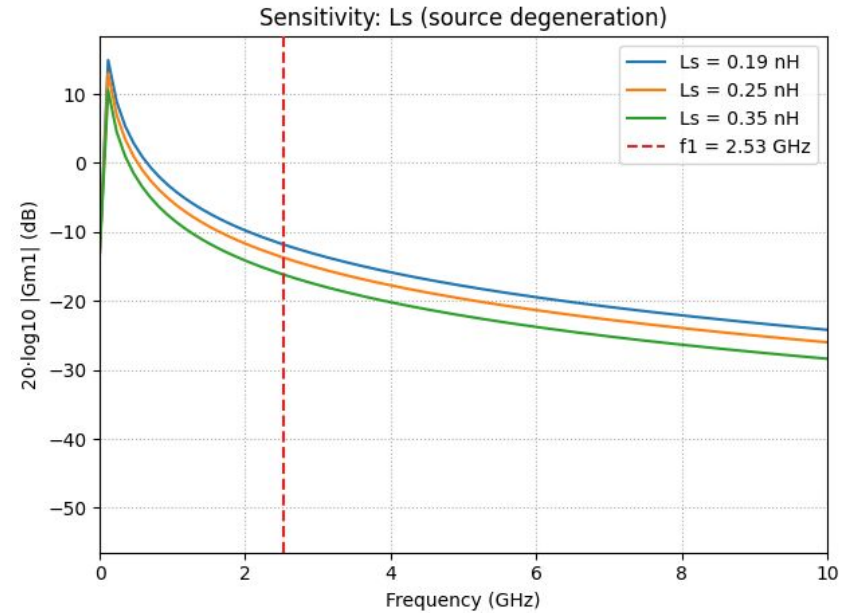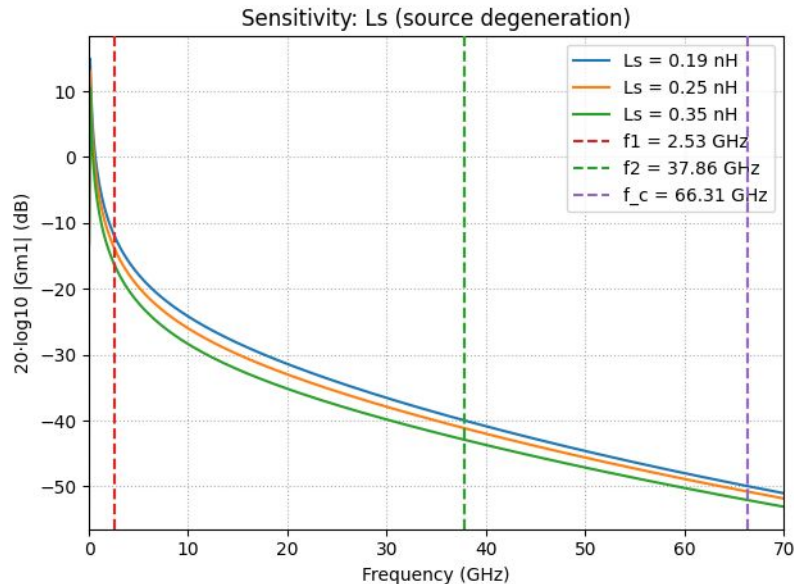- For Ls sweep gain drops as frequency increases
- Smaller Ls gives higher gain
- Larger Ls lower gain





With high frequency

- The first stage gain drops compare to the desired design frequency 4 - 8 GHz

Sensitivity to Lg Sweep

Plot shows

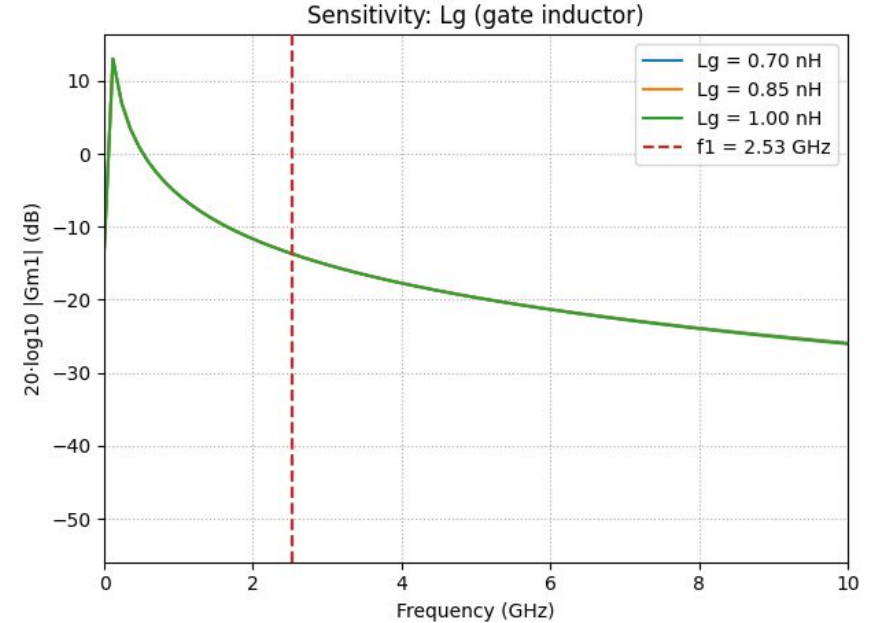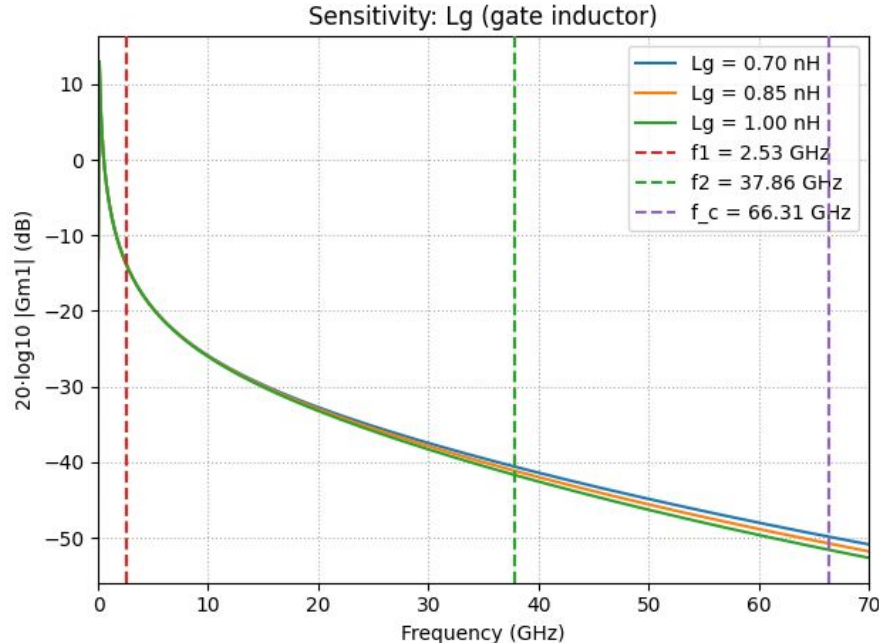- For Lg sweep gain drops as frequency increases
- 0 - 10 GHz, seems that they are perfectly overlapped



With high frequency

- The curve start separate
- lower Lg- higher gain
- Higher Lg - lower gain

Equation(4) Implementation

Resonant frequency and First stage gain

Resonant Frequencies - Transformer LC Tank

Let the node voltages across the tanks be $v_1(t), v_2(t)$ and the inductor branch currents be $i_1(t), i_2(t)$. For sinusoidal steady state with $s = j\omega$:

$$\begin{aligned} v_1 &= sL_{11} i_1 + sM i_2, \\ v_2 &= sM i_1 + sL_{12} i_2. \end{aligned} \quad (1)$$

Because the capacitors are in parallel with the inductors at each node, KCL gives

$$i_1 + C_{11}s v_1 = 0, \quad i_2 + C_{12}s v_2 = 0. \quad (2)$$

Eliminate i_1, i_2 from (1) using (2):

$$\begin{bmatrix} 1 - s^2 L_{11} C_{11} & -s^2 M C_{11} \\ -s^2 M C_{12} & 1 - s^2 L_{12} C_{12} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \mathbf{0}. \quad (3)$$

Nontrivial solutions require $\det(\cdot) = 0$:

$$(1 - s^2 L_{11} C_{11})(1 - s^2 L_{12} C_{12}) - s^4 M^2 C_{11} C_{12} = 0. \quad (4)$$

Let $x = s^2 = \omega^2$ and divide (4) by $L_{11} C_{11} L_{12} C_{12}$:

$$x^2(1 - k^2) - x\left(\frac{1}{L_{11} C_{11}} + \frac{1}{L_{12} C_{12}}\right) + \frac{1}{L_{11} C_{11} L_{12} C_{12}} = 0, \quad (5)$$

using $M^2 = k^2 L_{11} L_{12}$.

Write $\eta = \frac{L_{12} C_{12}}{L_{11} C_{11}}$ and multiply (5) by $L_{12} C_{12}$:


$$x^2(1 - k^2) L_{12} C_{12} - x(1 + \eta) + \frac{1}{L_{11} C_{11}} = 0. \quad (6)$$

Solve the quadratic in $x = \omega^2$:

$$\omega_{1,2}^2 = \frac{(1 + \eta) \mp \sqrt{(1 - \eta)^2 + 4\eta k^2}}{2 L_{12} C_{12} (1 - k^2)}. \quad (7)$$

Converting to frequency $f = \omega/(2\pi)$ gives
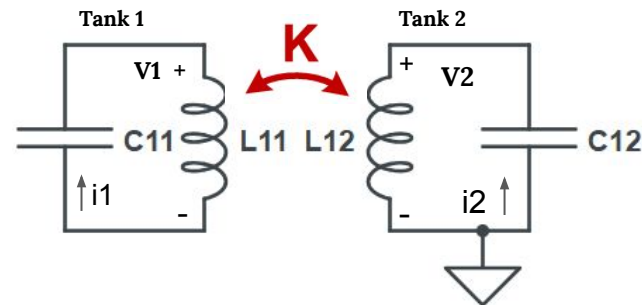
$$f_{1,2}^2 = \frac{1 + \eta \mp \sqrt{1 + \eta^2 - 2\eta(1 - 2k^2)}}{8\pi^2 L_{12} C_{12} (1 - k^2)} \quad (8)$$



- Primary Tank ($L_{11} \parallel C_{11}$)
- Secondary Tank ($L_{12} \parallel C_{12}$)
- Coupling factor $k \in [0, 1)$ by Mutual inductance $M = k\sqrt{L_{11}L_{12}}$
- Asymmetry parameter $\eta = (L_{12}C_{12})/(L_{11}C_{11})$

Resonant Frequencies - Transformer LC Tank

- The two resonant frequencies of the transformer-coupled LC tank are given by;

$$f_{1,2}^2 = \frac{1 + \eta \mp \sqrt{1 + \eta^2 - 2\eta(1 - 2k^2)}}{8\pi^2 L_{12}C_{12}(1 - k^2)}, \quad \eta = \frac{L_{12}C_{12}}{L_{11}C_{11}}, \quad k = \text{coupling}$$

- No coupling ($k=0$) and equal tanks ($\eta=1$) - Two independent LC tank
 - The formula collapses to

$$f_1 = \frac{1}{2\pi\sqrt{L_{12}C_{12}}}, \quad f_2 = \frac{1}{2\pi\sqrt{L_{11}C_{11}}}$$

- With coupling $K > 0$ - mode splitting into

$$f_1^2 = \frac{1}{4\pi^2 L_{12}C_{12}(1 + k)}, \quad f_2^2 = \frac{1}{4\pi^2 L_{12}C_{12}(1 - k)}$$

- In-phase mode f_1 - Lower frequency ($k+1$)
- Out-of-phase mode f_2 - Higher frequency ($k-1$)


Numerical values

- Using: $C_{11}=C_{12}= 0.4$ pF, $L_{11}= 1.9$ nH, $L_{12}=1.6$ nH, $k \approx 0.55$ and $\eta= 0.8421$. f_1 & f_2 becomes 4.82 & 9.01 GHz respectively.
- To match the paper exactly ($f_1 = 4.2$ GHz, $f_2 = 8.2$ GHz), both capacitors were scaled to $C_{11}=C_{12} \approx 0.518$ pF

Equation(4) Implementation - resonant frequency

Plot shows:

- **Blue curve (f1, lower mode):** In phase resonance frequency
 - As k increases, f_1 shifts from ~ 6 GHz to ~ 4 GHz
- **Orange curve (f2, upper mode):** out of phase resonant frq.
 - As k increases, f_2 shifts upward from ~ 6 GHz to ~ 19 GHz
- **Splitting behavior :** Two resonant frequencies move apart as coupling increases
 - At $k = 0$, the two modes are equal only if $\eta = 1$ (i.e., $L_{11}C_{11} = L_{12}C_{12}$). Otherwise they start separated
 - At $k = 0.55$, they are separated significantly
- **Target band (gray region 4.2 - 8.2 GHz):**
 - Target operating band of the LNA (the band we care about)
- **Coupling Coefficient K**
 - Shows how strongly the two inductors in the transformer tank are magnetically coupled
 - $K = 0$ - no coupling
 - Large k - stronger coupling, more separation between f_1 & f_2

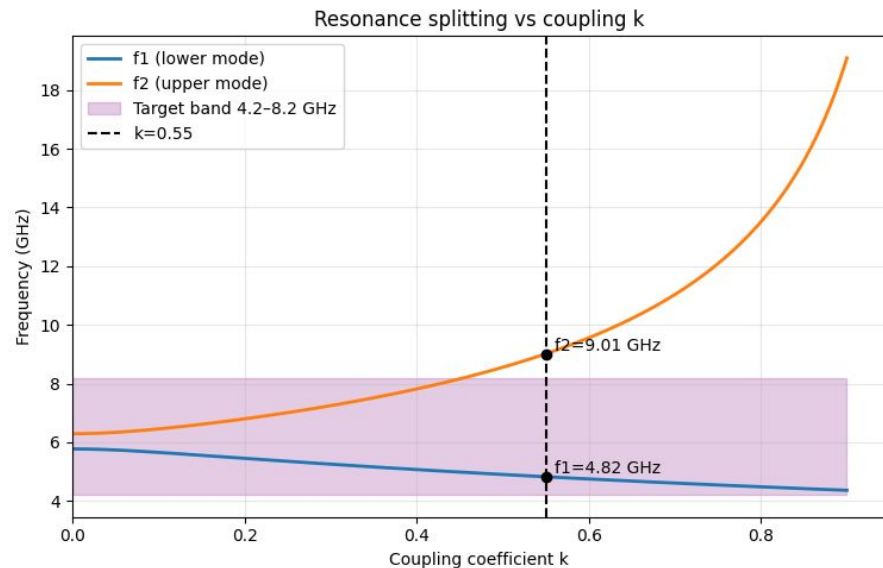


Parameter used:

$L_{11}=1.9\text{nH}, L_{12}=1.6\text{nH}, C_{11}=C_{12}=0.4\text{pF}, \eta=0.842, k=0.55$

Derivation of ZL

Set Up

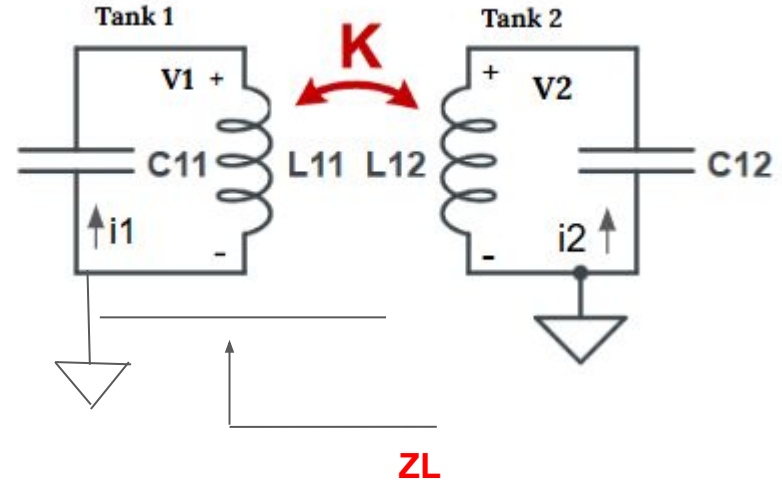

- Tank 1 = $(L11 \parallel C11)$
- Tank 2 = $(L12 \parallel C12)$
- Coupling factor $k \in [0,1)$ by $M = k\sqrt{L11L12}$
- Asymmetry parameter $\eta = (L12C12)/(L11C11)$

Derivation of ZL

Let the two parallel tanks be coupled via mutual inductance

$$M = k\sqrt{L_{11}L_{12}}, \quad \Delta_L = L_{11}L_{12} - M^2 = L_{11}L_{12}(1 - k^2).$$

Coupled inductor relation in frequency domain with node voltage v_1, v_2 and inductor branch currents i_1 and i_2

$$\begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = j\omega \underbrace{\begin{bmatrix} L_{11} & M \\ M & L_{12} \end{bmatrix}}_{\mathbf{L}} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} \Rightarrow \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \frac{1}{j\omega} \mathbf{L}^{-1} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix},$$

where the inverse of the 2×2 inductance matrix is

$$\mathbf{L}^{-1} = \frac{1}{\Delta_L} \begin{bmatrix} L_{12} & -M \\ -M & L_{11} \end{bmatrix}.$$


Shunt Capacitor currents

$$i_{C1} = j\omega C_{11}v_1, \quad i_{C2} = j\omega C_{12}v_2.$$

Since $Y = j\omega L^{-1}$ for an inductor branch,

$$\mathbf{Y}_L(\omega) = \frac{1}{j\omega \Delta_L} \begin{bmatrix} L_{12} & -M \\ -M & L_{11} \end{bmatrix}.$$

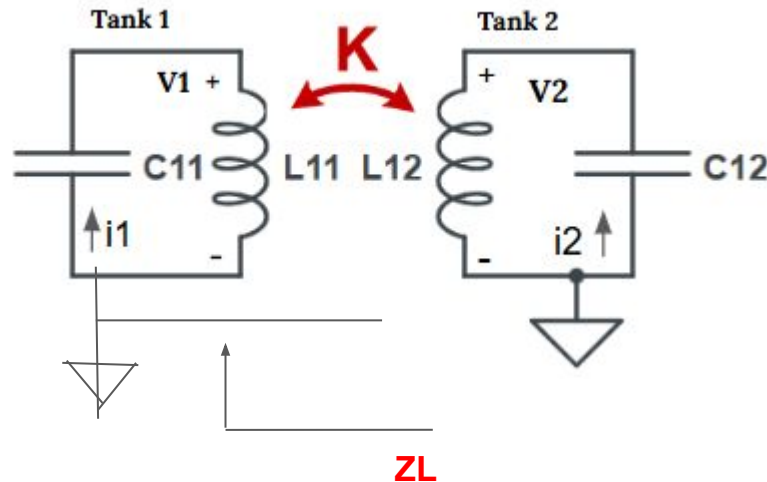Add shunts C and R_p to ground shunts at each node
add to the diagonal.



- Tank 1 = ($L_{11} \parallel C_{11}$)
- Tank 2 = ($L_{12} \parallel C_{12}$)
- Coupling factor $k \in [0, 1)$ by $M = k\sqrt{L_{11}L_{12}}$
- Asymmetry parameter $\eta = (L_{12}C_{12})/(L_{11}C_{11})$

Derivation of ZL continued . . .

$$\mathbf{Y}_{\text{sh}}(\omega) = \begin{bmatrix} G_1 + j\omega C_{11} & 0 \\ 0 & G_2 + j\omega C_{12} \end{bmatrix}$$

Thus the total two-node nodal admittance is

$$\mathbf{Y}(\omega) = \mathbf{Y}_{\text{sh}}(\omega) + \mathbf{Y}_L(\omega),$$

with entries

$$Y_{11}(\omega) = G_1 + j\omega C_{11} + \frac{L_{12}}{j\omega \Delta_L},$$

$$Y_{22}(\omega) = G_2 + j\omega C_{12} + \frac{L_{11}}{j\omega \Delta_L},$$

$$Y_{12}(\omega) = Y_{21}(\omega) = -\frac{M}{j\omega \Delta_L}.$$

For compactness the reactive parts can be written as;

$$X_1(\omega) = \omega C_{11} - \frac{L_{12}}{\omega \Delta_L}, \quad X_2(\omega) = \omega C_{12} - \frac{L_{11}}{\omega \Delta_L},$$

$$\text{so that } Y_{11} = G_1 + jX_1, Y_{22} = G_2 + jX_2, \text{ and } Y_{12} = +j \frac{M}{\omega \Delta_L}.$$

From Tank 1 and 2 circuit, nodal-admittance relationship for a two-node network is:

$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

Node 2 is floating, the input admittance is the Schur complement of Y_{22} :

$$\begin{cases} I_1 = Y_{11}V_1 + Y_{12}V_2, \\ I_2 = Y_{21}V_1 + Y_{22}V_2 = 0. \end{cases}$$

From this equation (since $I_2 = 0$), solve for V_2 :

$$V_2 = -Y_{22}^{-1}Y_{21}V_1.$$

Substituting this into I_1 gives

$$I_1 = Y_{11}V_1 + Y_{12}(-Y_{22}^{-1}Y_{21}V_1) = (Y_{11} - Y_{12}Y_{22}^{-1}Y_{21})V_1.$$

Therefore,

$$Y_{\text{in}} = Y_{11} - Y_{12}Y_{22}^{-1}Y_{21}$$

Derivation of ZL continued . . .

The block Y22 in the matrix Y . It represents the effective admittance seen at Node 1 after “eliminating” Node 2 mathematically.

$$Y_{in}(\omega) = Y_{11} - \frac{Y_{12}Y_{21}}{Y_{22}} = \frac{Y_{11}Y_{22} - Y_{12}^2}{Y_{22}}.$$

Therefore

$$Z_L(\omega) = \frac{1}{Y_{in}(\omega)} = \frac{Y_{22}}{Y_{11}Y_{22} - Y_{12}^2}.$$

Expand the denominator and substitute

First note

$$Y_{12}^2 = \left(j \frac{M}{\omega \Delta_L} \right)^2 = - \frac{M^2}{\omega^2 \Delta_L^2}.$$

Next,

$$Y_{11}Y_{22} = (G_1 + jX_1)(G_2 + jX_2) = G_1G_2 + j(G_1X_2 + G_2X_1) - X_1X_2.$$

Thus

$$Y_{11}Y_{22} - Y_{12}^2 = \left(G_1G_2 - X_1X_2 + \frac{M^2}{\omega^2 \Delta_L^2} \right) + j(G_1X_2 + G_2X_1).$$

Since $Y_{22} = G_2 + jX_2$, the final explicit result is

$$Z_L(\omega) = \frac{G_2 + jX_2}{\left(G_1G_2 - X_1X_2 + \frac{M^2}{\omega^2 \Delta_L^2} \right) + j(G_1X_2 + G_2X_1)}$$

With,

$$X_1(\omega) = \omega C_{11} - \frac{L_{12}}{\omega \Delta_L},$$

$$M = k\sqrt{L_{11}L_{12}},$$

$$G_1 = \frac{1}{R_{p1}},$$

$$X_2(\omega) = \omega C_{12} - \frac{L_{11}}{\omega \Delta_L},$$

$$\Delta_L = L_{11}L_{12} - M^2 = L_{11}L_{12}(1 - k^2),$$

$$G_2 = \frac{1}{R_{p2}}.$$

Derivation of ZL continued . . .

Substitute everything back again to get the final ZL

$$Z_L(\omega) = \frac{G_2 + j \left(\omega C_{12} - \frac{L_{11}}{\omega \Delta_L} \right)}{\left(G_1 G_2 - \left(\omega C_{11} - \frac{L_{12}}{\omega \Delta_L} \right) \left(\omega C_{12} - \frac{L_{11}}{\omega \Delta_L} \right) + \frac{M^2}{\omega^2 \Delta_L^2} \right) + j \left(G_1 \left(\omega C_{12} - \frac{L_{11}}{\omega \Delta_L} \right) + G_2 \left(\omega C_{11} - \frac{L_{12}}{\omega \Delta_L} \right) \right)}$$

Integrating Quality factor Q1 and Q2

For high-Q inductors, the series and parallel conversion is:

$$R_p(\omega) \approx \omega L Q \quad \Rightarrow \quad G(\omega) = \frac{1}{R_p(\omega)} \approx \frac{1}{\omega L Q}.$$

Then,

$$G_1(\omega) \approx \frac{1}{\omega L_{11} Q_1}, \quad G_2(\omega) \approx \frac{1}{\omega L_{12} Q_2},$$

With $G_1 = G_2 = 0$, parallel resonance occurs when $Y_{11}Y_{22} - Y_{12}^2 = 0$, leading to

$$\omega_{1,2}^2 = \frac{1 + \eta \mp \sqrt{1 + \eta^2 - 2\eta(1 - 2k^2)}}{2 L_{12} C_{12} (1 - k^2)}, \quad \eta \equiv \frac{L_{12} C_{12}}{L_{11} C_{11}}, \quad f_{1,2} = \frac{\omega_{1,2}}{2\pi}.$$

$$Y_{11}Y_{22} - Y_{12}^2 = \left(G_1 G_2 - X_1 X_2 + \frac{M^2}{\omega^2 \Delta_L^2} \right) + j (G_1 X_2 + G_2 X_1).$$

Derivation of ZL continued . . .

Zeros and poles: $Z_L(\omega) = \frac{G_2 + j \left(\omega C_{12} - \frac{L_{11}}{\omega \Delta_L} \right)}{\left(G_1 G_2 - \left(\omega C_{11} - \frac{L_{12}}{\omega \Delta_L} \right) \left(\omega C_{12} - \frac{L_{11}}{\omega \Delta_L} \right) + \frac{M^2}{\omega^2 \Delta_L^2} \right) + j \left(G_1 \left(\omega C_{12} - \frac{L_{11}}{\omega \Delta_L} \right) + G_2 \left(\omega C_{11} - \frac{L_{12}}{\omega \Delta_L} \right) \right)} = \frac{N(s)}{D(s)}$

Zeros

$$Y_{22}(s) = \bar{G}_2 + s C_{12} + \frac{L_{11}}{\Delta_L} \frac{1}{s}, \quad \Delta_L \equiv L_{11} L_{12} - M^2, \quad M = k \sqrt{L_{11} L_{12}}.$$

$$N(s) = s^2 Y_{22}(s) = C_{12} s^3 + \bar{G}_2 s^2 + \frac{L_{11}}{\Delta_L} s.$$

Therefore the zeros of $Z_L(s)$ are the roots of $N(s) = 0$:

$$s = 0, \quad C_{12} s^2 + \bar{G}_2 s + \frac{L_{11}}{\Delta_L} = 0.$$

Solving the quadratic gives the two finite zeros

$$s_{z1,2} = \frac{-\bar{G}_2 \pm \sqrt{\bar{G}_2^2 - 4 C_{12} \frac{L_{11}}{\Delta_L}}}{2 C_{12}} = -8.0219 \times 10^9 \pm j 4.1566 \times 10^{10} \text{ rad/s}.$$

$$z_0 = 0, \quad z_{1,2} = -8.022 \times 10^9 \pm j 4.1566 \times 10^{10} \text{ rad/s}, \quad f_z = \frac{|\text{Im } z|}{2\pi} = 6.616 \text{ GHz}.$$

$$\omega_{\text{ref}} = \frac{\omega_1 + \omega_2}{2} \Rightarrow f_{\text{ref}} = \frac{f_1 + f_2}{2}.$$

With band ends $f_1 = 4.20 \text{ GHz}$, $f_2 = 8.20 \text{ GHz}$:

$$f_{\text{ref}} = \frac{4.2+8.2}{2} = 6.20 \text{ GHz}.$$

Poles

$$Y_{11}(s) = \bar{G}_1 + s C_{11} + \frac{L_{12}}{\Delta_L} \frac{1}{s},$$

$$Y_{22}(s) = \bar{G}_2 + s C_{12} + \frac{L_{11}}{\Delta_L} \frac{1}{s}, \quad \Delta_L = L_{11}L_{12} - M^2,$$

$$Y_{12}(s) = -\frac{M}{\Delta_L} \frac{1}{s},$$

Substitute constants ($L_{11} = 1.9 \text{ nH}$, $L_{12} = 1.6 \text{ nH}$, $C_{11} = C_{12} = 0.5 \text{ pF}$, $k = 0.55$).

$$\Delta_L = (1 - k^2)L_{11}L_{12} = 2.12 \times 10^{-18} \text{ H}^2, \quad \frac{L_{11}}{\Delta_L} = 8.9606 \times 10^8 \text{ s}^{-2},$$

$$\bar{G}_1 = \frac{1}{2\pi f_{\text{ref}}L_{11}Q_1} = 1.6476 \times 10^{-3} \text{ S } (Q_1 = 8.2), \quad \bar{G}_2 = \frac{1}{2\pi f_{\text{ref}}L_{12}Q_2} = 8.0219 \times 10^{-3} \text{ S } (Q_2 = 2).$$

Poles from the denominator $D(s) = s^2(Y_{11}Y_{22} - Y_{12}^2)$.

$$D(s) = (C_{11}C_{12})s^4 + (\bar{G}_1C_{12} + \bar{G}_2C_{11})s^3 + \left(\bar{G}_1\bar{G}_2 + \frac{C_{11}L_{11} + C_{12}L_{12}}{\Delta_L}\right)s^2 + \frac{\bar{G}_1L_{11} + \bar{G}_2L_{12}}{\Delta_L}s + \frac{1}{\Delta_L}.$$

Coeffs: $a_4 = 2.50 \times 10^{-25}$, $a_3 = 4.8348 \times 10^{-15}$, $a_2 = 8.3853 \times 10^{-4}$, $a_1 = 7.5295 \times 10^6$,
 $a_0 = 4.7161 \times 10^{17}$.

Roots $D(s) = 0$:

$$p_{1,2} = -5.2378 \times 10^9 \pm j 4.9821 \times 10^{10} \text{ rad/s}, \quad p_{3,4} = -4.4317 \times 10^9 \pm j 2.7056 \times 10^{10} \text{ rad/s}.$$

Imaginary parts $\Rightarrow f_1 = 7.929 \text{ GHz}$, $f_2 = 4.306 \text{ GHz}$.


$|Z_L|$ vs Frequency plot

Key Observations:

- The plot shows the magnitude of the load impedance $|Z_L|$, drive from the coupled-tank network:

$$Z_L(f) = \frac{1}{Y_{11} - \frac{Y_{12}^2}{Y_{22}}}$$

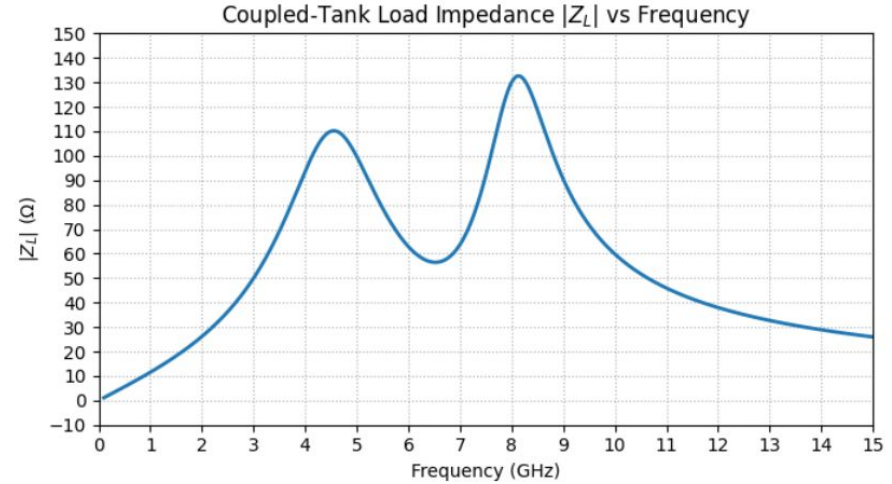- Two resonance peak appears:
 - $f_1 \approx 4.2$ GHz — lower-mode resonance.
 - $f_2 \approx 8.2$ GHz — upper-mode resonance.
- The valley around 6–7 GHz arises from coupling-induced mode splitting between even and odd tank modes




Parameter Setup:

- $L_{11} = 1.9$ nH, $L_{12} = 1.6$ nH, $C_{11} = C_{12} = 0.5$ pF, $k = 0.55$
- $Q_1 = 8.2$, $Q_2 = 2.0$

$|Z_L|$ vs Frequency plot

What Changes What:


- Increase $k \rightarrow$ widens the separation between f_1 and f_2 (stronger mode split).
- Decrease $k \rightarrow$ merges the peaks into a single resonance.
- Increase Q_1 or $Q_2 \rightarrow$ raises corresponding peak height and sharpness.
- Increase C_{12} or $L_{12} \rightarrow$ shifts both peaks to lower frequencies.
- Increase losses (lower Q) \rightarrow flattens peaks and widens bandwidth.

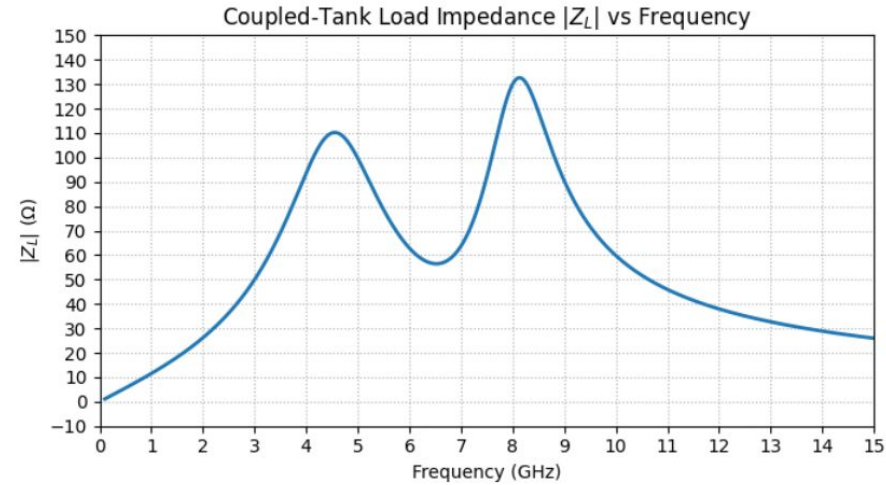

Parameter Setup:


- $L_{11} = 1.9$ nH, $L_{12} = 1.6$ nH, $C_{11} = C_{12} = 0.4$ pF, $k = 0.55$
- $Q_1 = 8.2$, $Q_2 = 2.0$

Effective Transconductance Magnitude $|G_{m1}|$ vs Frequency

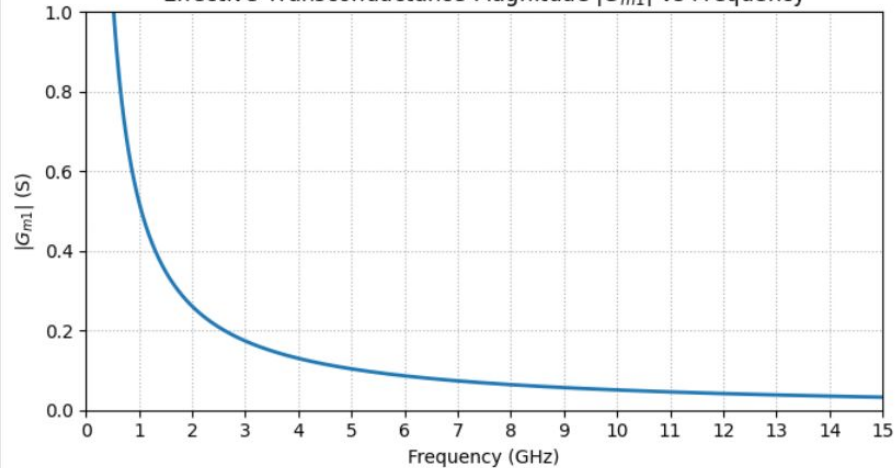


X

Coupled-Tank Load Impedance $|Z_L|$ vs Frequency

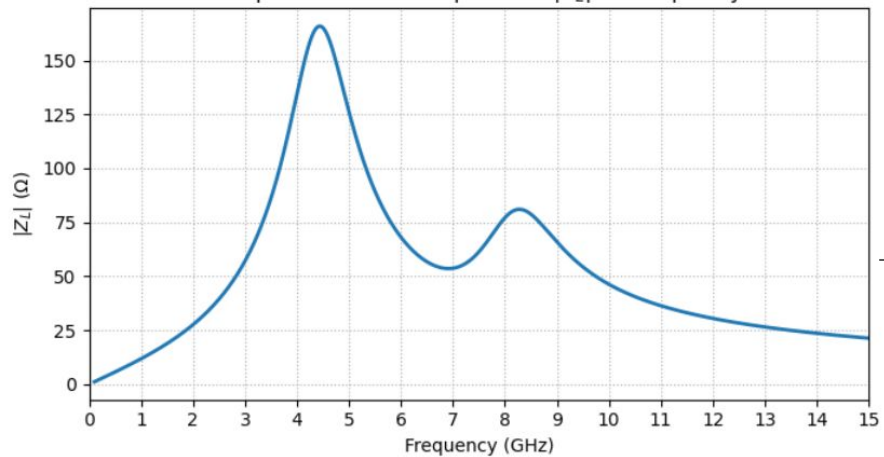

With $Q_1=8.2, Q_2=2$


First-Stage Gain $|A_{v1}|$ vs Frequency

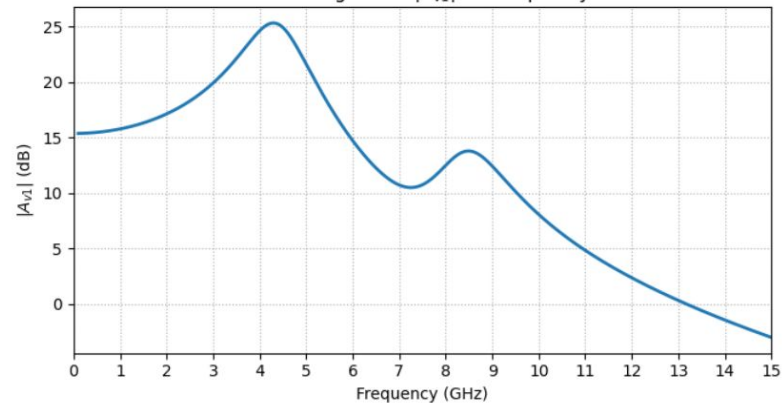

=


When C_{11} and C_{12} are not equal
 $K = 0.58$

Effective Transconductance Magnitude $|G_{m1}|$ vs Frequency

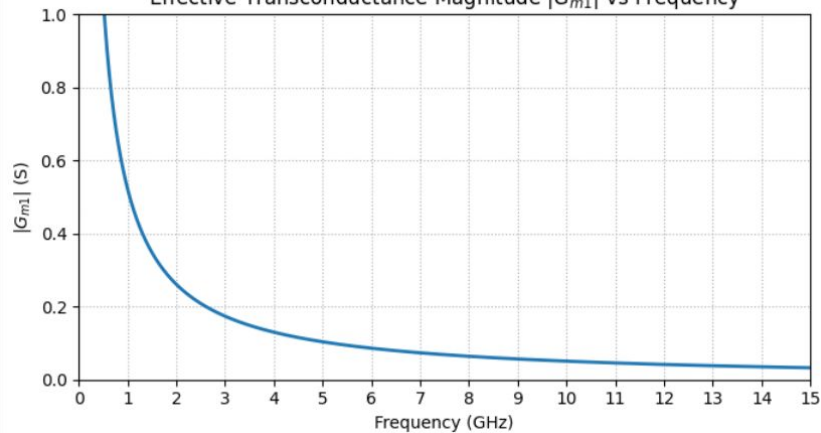

X


Coupled-Tank Load Impedance $|Z_L|$ vs Frequency

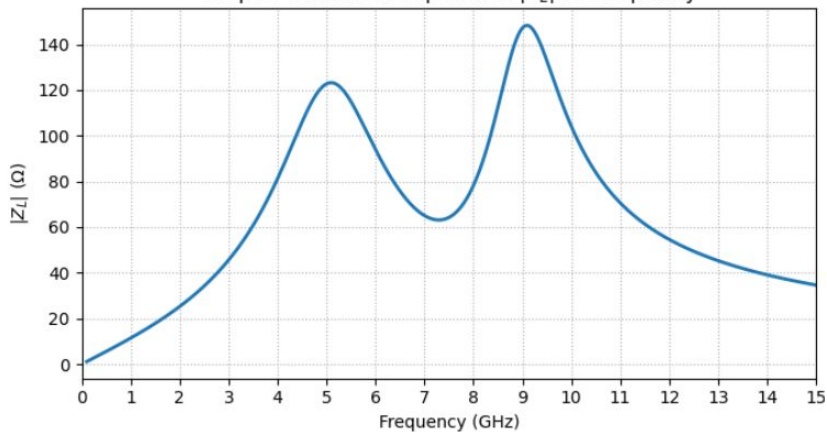

=

With $Q_1=8.2, Q_2=2$

First-Stage Gain $|A_{v1}|$ vs Frequency

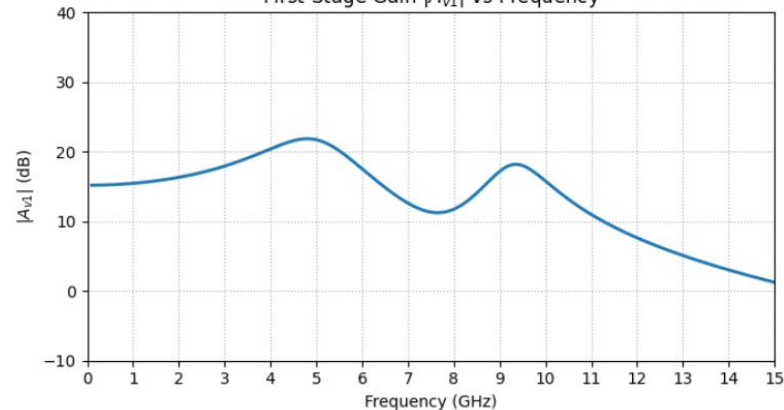

When C_{11} and C_{12} are equal
 $K = 0.55$

First Stage Gain

- The plot shows the simulated first-stage voltage gain magnitude

$$|A_{v1}(f)| = |G_{m1}(f)| \times |Z_L(f)|$$

over the 0–15 GHz range.


- Two gain peaks appear at:
 - $f_1 \approx 4.2$ GHz — lower-mode resonance
 - $f_2 \approx 8.2$ GHz — upper-mode resonance

These originate from the coupled LC tanks at the drain.

- The valley between ~ 6 – 7 GHz results from mode splitting and mutual coupling (parameter k).

Interpretation:

- Peak 1 (~ 4.2 GHz):** Dominated by tank 1 resonance and large $|Z_L|$. Limited by Q_1 and finite $|G_{m1}|$.
- Valley (~ 6 – 7 GHz):** Occurs due to coupling-induced impedance splitting between even and odd tank modes.
- Peak 2 (~ 8.2 GHz):** Driven by tank 2 resonance. Smaller because $|G_{m1}|$ rolls off at high frequency.

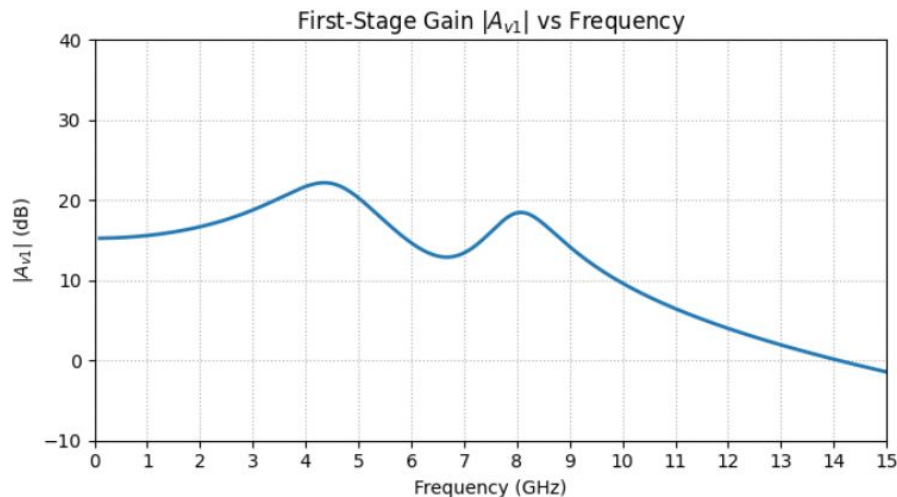

Parameter Setup:

- $L_{11} = 1.9$ nH, $L_{12} = 1.6$ nH, $C_{11} = C_{12} = 0.4$ pF, $k = 0.55$
- $Q_1 = 8.2$, $Q_2 = 2.0$
- $g_{m1} = 0.22$ S, $g_{m2} = 0.10$ S
- $L_s = 0.25$ nH, $L_g = 0.85$ nH, $R_s = 50$ Ω


First Stage Gain

What Changes What:


- Increase $Q_1 \rightarrow$ raises f_1 peak amplitude (sharper resonance).
- Decrease $Q_1 \rightarrow$ lowers f_1 peak; flattens the valley.
- Increase $Q_2 \rightarrow$ raises f_2 peak amplitude.
- Increase $k \rightarrow$ widens peak separation (larger mode split).
- Increase C_{12} or $L_{12} \rightarrow$ shifts f_2 lower, affects symmetry.
- Increase g_{m1} or reduce $L_s \rightarrow$ raises overall gain level.

Conclusion:

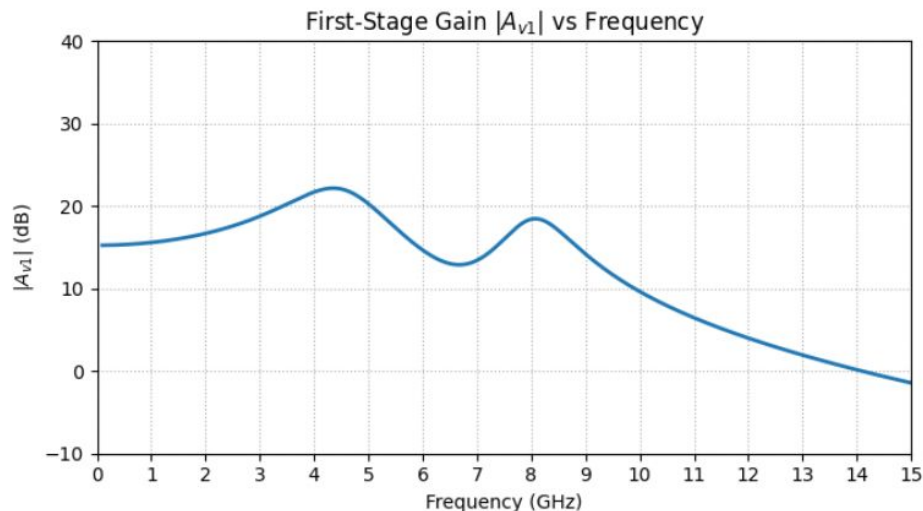- Confirms the broadband dual-resonance behavior of the coupled tanks.
- Gain remains > 11 dB across 3.7–9 GHz, consistent with the paper's trend.
- Tuning Q_1/Q_2 , k , and C_{12} allows fine control of bandwidth and peak symmetry.



First stage gain with Poles and Zeros

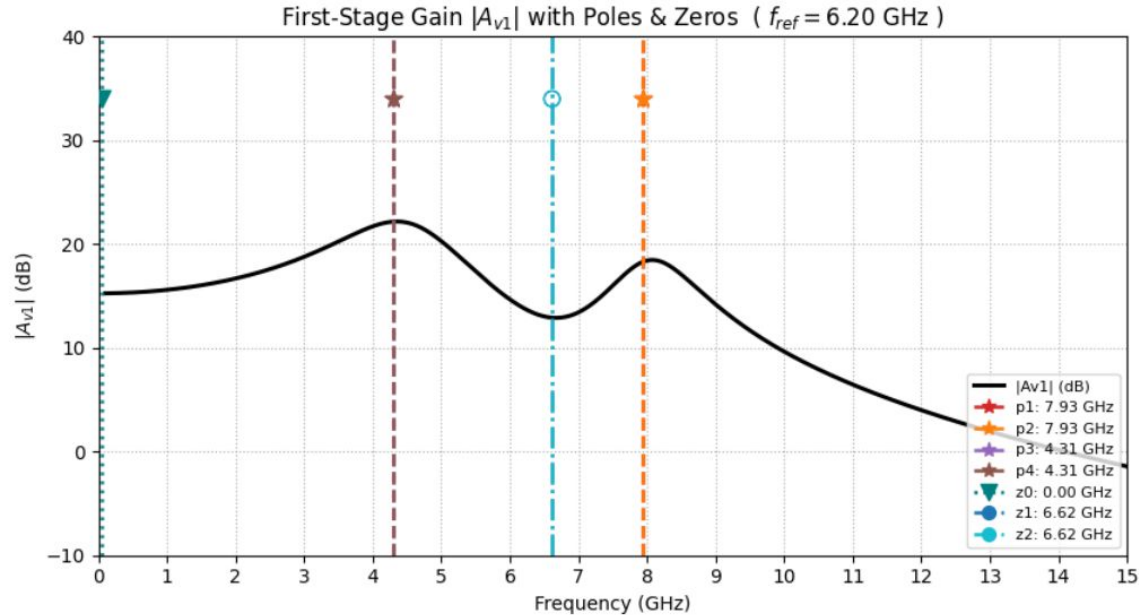

$f_{ref} = 6.200$ GHz

Poles (s-plane):

p1:	$-5.237844e+09$	$+ j 4.982125e+10$	rad/s	-->	$ Im /(2\pi) = 7.929298$ GHz
p2:	$-5.237844e+09$	$- j 4.982125e+10$	rad/s	-->	$ Im /(2\pi) = 7.929298$ GHz
p3:	$-4.431713e+09$	$+ j 2.705643e+10$	rad/s	-->	$ Im /(2\pi) = 4.306165$ GHz
p4:	$-4.431713e+09$	$- j 2.705643e+10$	rad/s	-->	$ Im /(2\pi) = 4.306165$ GHz

Zeros (s-plane):

z0:	$0.000000e+00$	$+ j 0.000000e+00$	rad/s	-->	0.000000 GHz
z1:	$-8.021923e+09$	$+ j 4.156637e+10$	rad/s	-->	$ Im /(2\pi) = 6.615494$ GHz
z2:	$-8.021923e+09$	$- j 4.156637e+10$	rad/s	-->	$ Im /(2\pi) = 6.615494$ GHz

Implementation of equation 5 & 6

Input Impedance Match Analysis

Derivation of equation(5,6)

KCL at G; Gate current:

$$I_{in} = j\omega C_{gs1}(V_g - V_s) + j\omega C_{gd1}(V_g - V_d), \quad Z_{in} = \frac{V_g}{I_{in}}.$$

KCL at D, solve Vd: sum of current leaving D = 0

$$\frac{V_d}{Z_D} + sC_{gd1}(V_d - V_g) + g_{ds1}(V_d - V_s) + g_{m1}(V_g - V_s) = 0.$$

Group by node voltage and define; $A \equiv \frac{1}{Z_D} + sC_{gd1} + g_{ds1}$.

$$V_d = \frac{(sC_{gd1} - g_{m1})V_g + (g_{ds1} + g_{m1})V_s}{A}.$$

KCL at S, solve Vs/Vg: current leaving S

$$\frac{V_s}{sL_S} + sC_{gs1}(V_s - V_g) + g_{ds1}(V_s - V_d) - g_{m1}(V_g - V_s) = 0.$$

Define

$$B \equiv \frac{1}{sL_S} + sC_{gs1} + g_{ds1} + g_{m1},$$

so that

$$B V_s = (sC_{gs1} + g_{m1})V_g + g_{ds1}V_d.$$

Substitute Vd and solve for Vs/Vg; $\frac{V_s}{V_g} = \frac{A(sC_{gs1} + g_{m1}) + g_{ds1}(sC_{gd1} - g_{m1})}{AB - g_{ds1}(g_{ds1} + g_{m1})}$

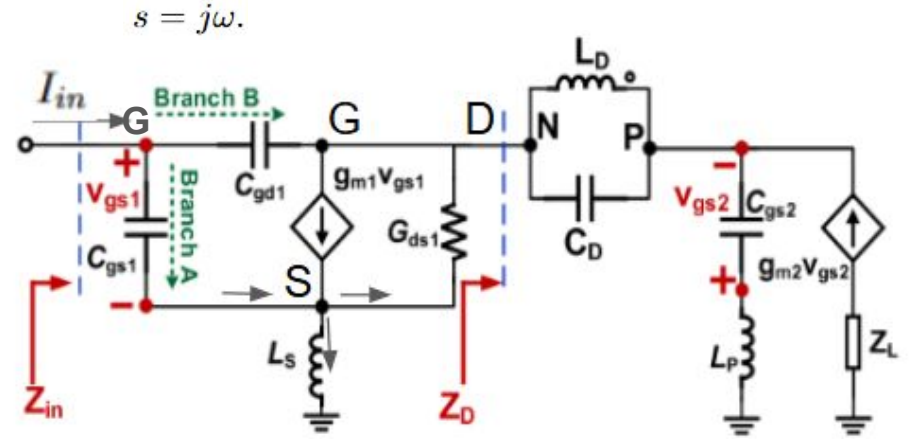


Fig. 3. Small-signal equivalent circuit of the input stage for Z_{in} derivation.

Branch currents leaving the nodes

$$\begin{aligned} i_{gs1} &= sC_{gs1}(V_g - V_s), & i_{gd1} &= sC_{gd1}(V_g - V_d), \\ i_{ds1} &= g_{ds1}(V_d - V_s), & i_{gm1, \text{from } D} &= g_{m1}(V_g - V_s), \\ i_{Z_D} &= \frac{V_d}{Z_D}, & i_{L_S} &= \frac{V_s}{sL_S}. \end{aligned}$$

Derivation of equation(5,6) continue . . .

For compactness, denote $r = V_s/V_g$ and $r = N_r/D_r$ with

$$N_r = A(sC_{gs1} + g_{m1}) + g_{ds1}(sC_{gd1} - g_{m1}), \quad D_r = AB - g_{ds1}(g_{ds1} + g_{m1})$$

From KCL@ D, express it as V_d/V_g

$$\frac{V_d}{V_g} = \frac{(sC_{gd1} - g_{m1}) + (g_{ds1} + g_{m1})r}{A}$$

Input current and Z_{in} ,

$$I_{in} = j\omega C_{gs1}(V_g - V_s) + j\omega C_{gd1}(V_g - V_d), \quad Z_{in} = \frac{V_g}{I_{in}}.$$

Then divided by V_g , use $r = V_s/V_g$ and V_d/V_g

$$\frac{I_{in}}{V_g} = sC_{gs1}(1 - r) + sC_{gd1} \left[1 - \frac{(sC_{gd1} - g_{m1}) + (g_{ds1} + g_{m1})r}{A} \right]$$

Write each part over its natural denominator and combine:

$$\frac{I_{in}}{V_g} = sC_{gs1} \frac{D_r - N_r}{D_r} + sC_{gd1} \frac{A - (sC_{gd1} - g_{m1}) - (g_{ds1} + g_{m1})r}{A}$$

With $r = N_r/D_r$ and common denominator AD_r :

$$\frac{I_{in}}{V_g} = \frac{sC_{gs1}A(D_r - N_r) + sC_{gd1}[AD_r - A(sC_{gd1} - g_{m1})D_r - (g_{ds1} + g_{m1})N_r]}{AD_r}$$

Therefore Z_{in} ,

$$Z_{in} = \frac{V_g}{I_{in}} = \frac{AD_r}{sC_{gs1}A(D_r - N_r) + sC_{gd1}[AD_r - A(sC_{gd1} - g_{m1})D_r - (g_{ds1} + g_{m1})N_r]}$$

Substitute back, $s = j\omega$

$$N_r = A(sC_{gs1} + g_{m1}) + g_{ds1}(sC_{gd1} - g_{m1}), \quad D_r = AB - g_{ds1}(g_{ds1} + g_{m1})$$

To simplify introduce T and CT

$$T = sL_S(g_{m1} + sC_{gs1} + g_{ds1}), \quad C_T = C_{gs1} + \frac{g_{ds1}}{s},$$

expand $A = \frac{1}{Z_D} + sC_{gd1} + g_{ds1}$ and $B = \frac{1}{sL_S} + sC_{gs1} + g_{ds1} + g_{m1}$, and simplify to obtain

$$Z_{in} = \frac{(1 + sC_{gd1}Z_D)(1 + T) + Z_Dg_{ds1}(1 - \omega^2L_SC_{gs1})}{j\omega \left\{ (Z_D + sL_S)[g_{ds1}C_T + C_{gd1}(g_{m1} + sC_{gs1})] + C_T \right\}}$$

where:

- $C_T = C_{gs1} + C_{gd1}$ (note: the document states $C_T = C_{gs1} + g_{ds1}$, but this appears to be a typographical error, as the units do not match; the correct term is likely $C_{gs1} + C_{gd1}$ for dimensional consistency),

Derivation of equation(5,6) continue . . .

Drain looking-In Impedance ZD

- From node D (M1 drain), the right network consists of: Series peaking inductor L_P into the common-gate input of M2, whose shunt input is $g_{m2} \parallel j\omega C_{gs2}$, giving

$$Z_{CG+L_P} = j\omega L_P + \frac{1}{g_{m2} + j\omega C_{gs2}} = \frac{1 + j\omega L_P g_{m2} - \omega^2 L_P C_{gs2}}{g_{m2} + j\omega C_{gs2}} = \frac{1 - \omega^2 L_P C_{gs2}}{g_{m2} + j\omega C_{gs2}}$$

Note : - The small term **$j\omega L_P g_{m2}$** is typically negligible and omitted in the paper

- Parallel tank $L_D \parallel C_D$

$$Z_{L_D \parallel C_D} = \frac{j\omega L_D}{1 - \omega^2 L_D C_D}$$

- Summing Everything together Gives :

$$Z_D = \frac{1 - \omega^2 L_P C_{gs2}}{g_{m2} + j\omega C_{gs2}} + \frac{j\omega L_D}{1 - \omega^2 L_D C_D}$$

Paper assumptions used for these plots

- **Equations:** Eq. (5) for Z_{in} and simplified Eq. (6) for Z_D :

$$C_T = C_{gs1}, \quad T = j\omega L_S(g_{m1} + j\omega C_{gs1} + G_{ds1}),$$

$$Z_D(\omega) \approx \frac{1}{g_{m2}} + \frac{j\omega L_D}{1 - \omega^2 L_D C_D}.$$

- **Neglected in Eq. (6):** C_{gs2} and L_P , under the paper's conditions $g_{m2} \gg \omega C_{gs2}$ and $\omega^2 L_P C_{gs2} \ll 1$.
- **No explicit losses:** ideal L/C (infinite Q); no shunt/series damping (R_p , R_{pad}), no gate resistance R_g , no pad/bond/parasitics.
- **Reference impedance:** $Z_0 = 50 \Omega$.
- **Device constants :** $C_{gs1} = 0.24$ pF, $C_{gd1} = 90$ fF, $G_{ds1} = 33$ mS, $g_{m1} = 0.22$ S.
- **Port modeling:** single-ended input with series L_G included explicitly.

Common device/constants (used in both Fig. 4a & 4b)

Calculated (Eq. 5–6), $CT = C_{gs1}$, no explicit loss (no R_p , no series R)

Parameter	Paper (units)	Used (units)	Offset
$CT = C_{gs1}$	0.24 pF	0.24 pF	0%
C_{gd1}	90 fF	90 fF	0%
$gm1$	0.22 S	0.22 S	0%
G_{ds1}	33 mS	33 mS	0%
Z_0 (for S_{11})	50 Ω	50 Ω	0%
C_{gs2} (Eq. 6)	not used (assumed ≈ 0)	0	N/A
LP (Eq. 6)	not used (assumed ≈ 0)	0	N/A

Case: $LD = 1$ nH (green “Cal.”)			
Parameter	Paper (units)	Used (units)	Offset
LG	0.85 nH	0.85 nH	0%
LS	0.25 nH	0.25 nH	0%
LD	1.00 nH	1.00 nH	0%
CD	2.5 pF	2.5 pF	0%
$gm2$	0.10 S	0.10 S	0%

Eq.(6) simplified per paper: no C_{gs2} , LP



Common device/constants (used in both Fig. 4a & 4b)

Case: LD = 100 nH (blue “Cal.”)			
Parameter	Paper (unit)	Used (unit)	Offset
LG	0.90 nH	0.90 nH	0%
LS	0.19 nH	0.19 nH	0%
LD	100 nH	100 nH	0%
CD	2.9 pF	2.9 pF	0%
gm2	not published	0.05 S (Assumed)	N/A

Notes

- For the 100 nH case the paper doesn't publish gm2; they state LG,LS,CD were set for optimum S11 and gm2 was adjusted. I used 0.05 S as the nominal value when plotting.
- Eq. (6) was used in its simplified form (neglecting Cgs2 and LP), per the paper's stated assumptions.

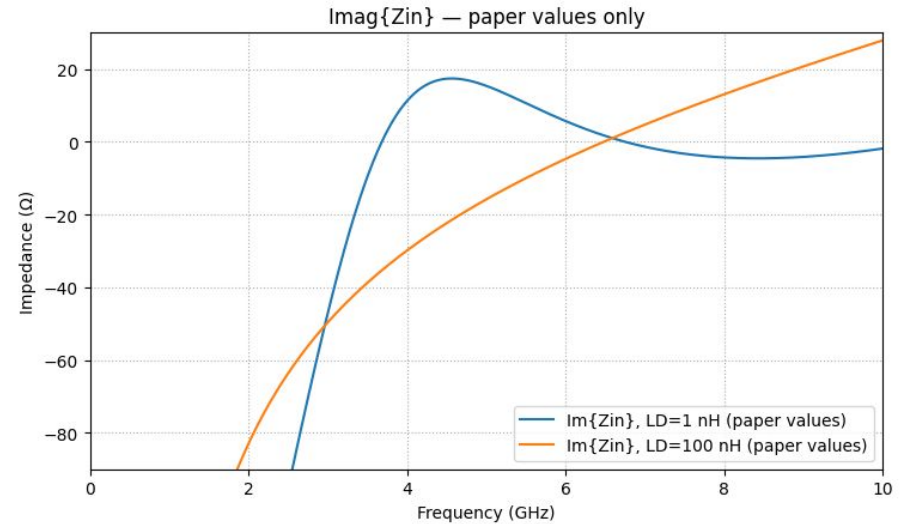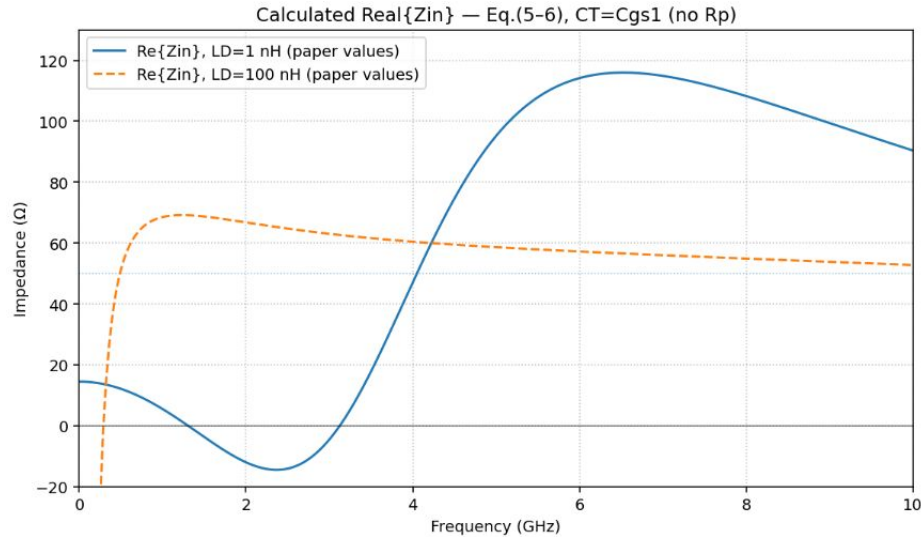Plot with only Eqn (5) & (6) and papers assumption



For LD=1 nH
Im = 0, at ~ 4GHZ, Re ~45 Ohm


For LD=1 nH
Im = 0, at ~ 4GHZ

Dip location: find the zero of Im{Zin}

Dip depth : Evaluate $R = \text{Re}\{Z_{in}\}$ at that frequency used

$$|S_{11}|_{\text{dip}} = \left| \frac{R - 50}{R + 50} \right|, \quad \text{Depth (dB)} = 20 \log_{10} \left| \frac{R - 50}{R + 50} \right|$$

|S11|

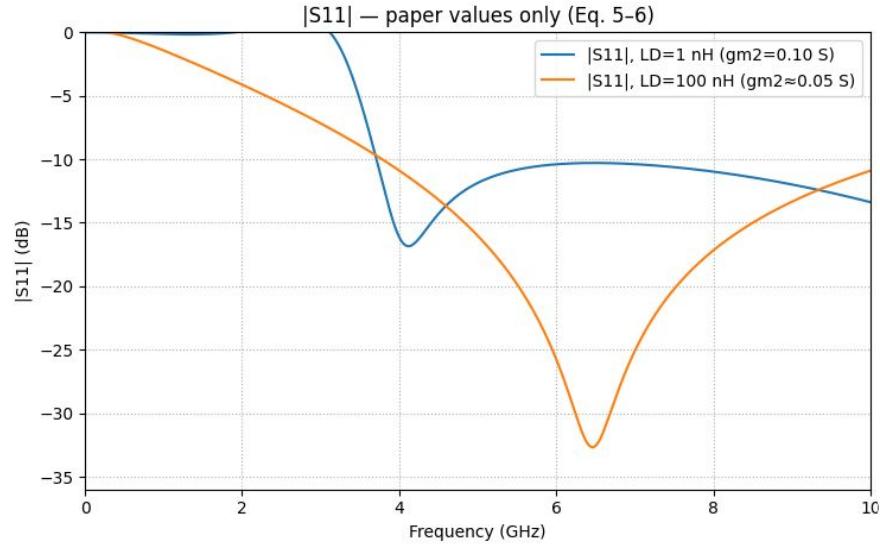

For LD = 1 nH

R ~ 45 Ohm

$20 \log_{10}^{(40-50)/(40+50)} \approx -17 \text{ dB}$

|s11| dip is ~ -17 dB

Change LS,LG, and gm2 to see what's happening

Calculated (Eq. 5–6), $CT = C_{gs1}$, used R_p .

Parameter	Paper value (unit)	Used with R_p (unit)	Offset
Cgs1	0.24 pF	0.24 pF	0%
Cgd1	90 fF	90 fF	0%
Gds1	33 mS	33 mS	0%
gm1	0.22 S	0.22 S	0%

Case: LD = 100 nH (blue “Cal.”)			
Parameter	Paper value (unit)	Used (R_p) (unit)	Offset
LG	0.85 nH	0.85 nH	0%
LS	0.25 nH	0.25 nH	0%
LD	1.00 nH	1.00 nH	0%
CD	2.5 pF	2.5 pF	0%
gm2	0.10 S	0.10 S	0%


Change some variables to see what's happening

Case: LD = 1 nH (“Cal.”)			
Parameter	Paper value (unit)	Used (Rp) (unit)	Offset
LG	0.85 nH	0.84nH	-1.2 %
LS	0.25 nH	0.34nH	+36 %
LD	1.00 nH	1.00nH	0%
CD	2.5 pF	2.6 pF	+4%
gm2	0.1 S	0.1 S	0%

As The paper stated that “Actually, as long as $\text{Re}\{Z_{in}\}$ is positive, the circuit is stable.” so, to lift up $\text{Re}\{Z_{in}\}$ above 0, at LD = 1nH some parameters need to be swept which are LS, LG, and gm2


Impedance vs Frequency plot with parallel Rp

Real{Zin} — Eq.(5-6) with CT=Cgs1, Rp across LD||CD

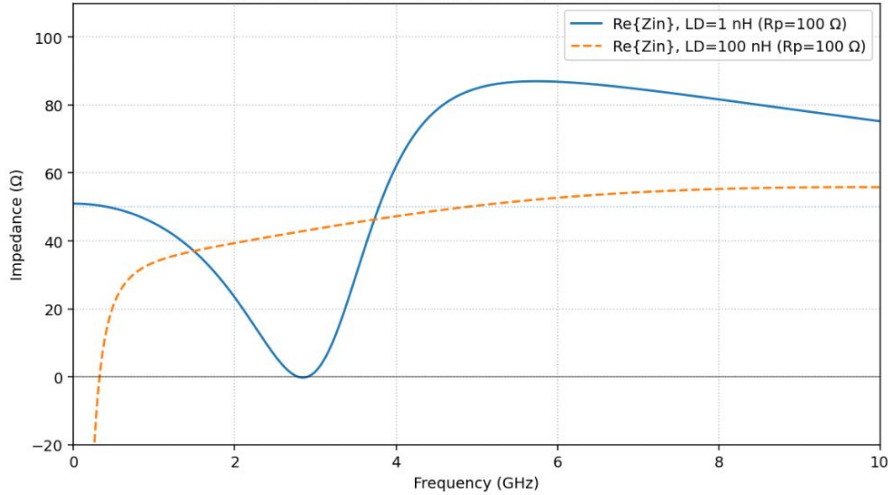

- At $\text{Im}=0$, if $R > 50 \Omega$ (dip too shallow) $\rightarrow \uparrow \text{gm}_2$ or $\downarrow \text{LS}$
- At $\text{Im}=0$, if $R < 50 \Omega$ (over-deep/narrow) $\rightarrow \downarrow \text{gm}_2$ or $\uparrow \text{LS}$
- If Im above 0 (near dip) $\rightarrow \uparrow \text{gm}_2$; if below 0 $\rightarrow \downarrow \text{gm}_2$
- R_p and gm_2 , moves both Re and Im part up and down


Imag{Zin} — Eq.(5-6) with CT=Cgs1, Rp across LD||CD

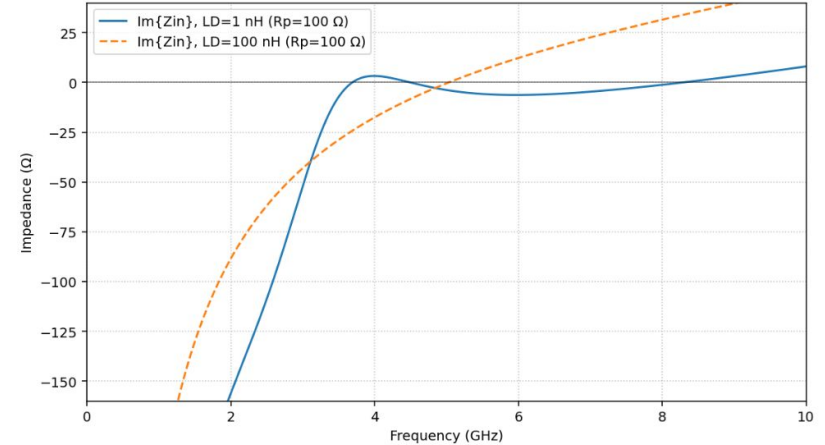

- Im curve sits below 0 \rightarrow decrease gm_2 a bit.
- Im curve sits above 0 around the dip \rightarrow increase gm_2 a bit

Large L_s and Lower gm_2 helps to ensure $\text{Re}\{Z_{in}\} > 0$

|S11|

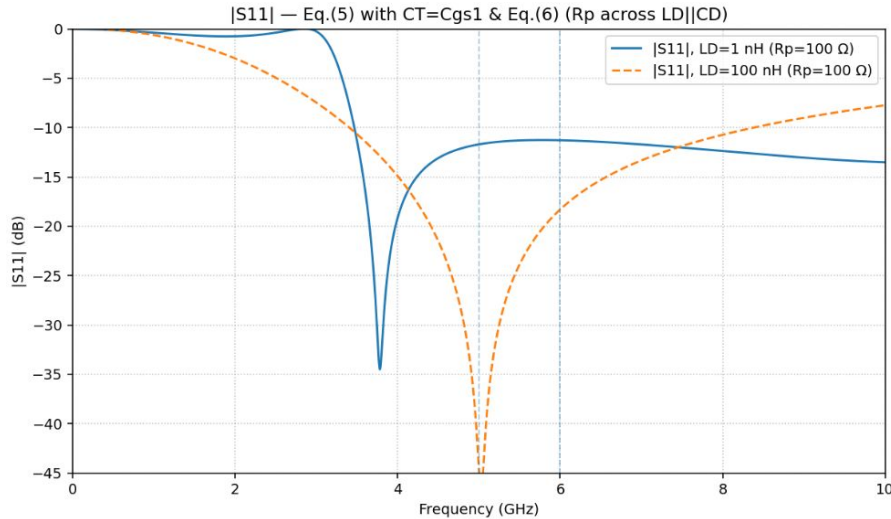

Shift dip left/right:

- $\uparrow CD, \uparrow LG$ move left (\leftarrow)
- $\downarrow CD, \downarrow LG$ move to the right (\rightarrow)

- Use LG and CD (plus C_{gs1} if needed) to place the dip.
- Decrease Lg or CD dip too low in frequency
- Increase Lg or CD dip too high in frequency
- Use LS, gm1, gm2 to set depth (via the real plateau).
- Use R_p / finite Q to control Q and stability (broaden/shallow), with minimal frequency pull.

Keep Parameters consistency throughout first stage design

A

First stage design constants from equation(3) - (6) used these base device parameters.

- $gm1 = 0.22$, # S
- $gm2 = 0.10$, # S
- $Cgs1 = 0.24e-12$, # F
- $Cgd1 = 90e-15$, # F
- $Gds1 = 33e-3$, # S

B

On top of those constants from A, only equation (3),(5), and (6) depends on LS,LG

- $Lg = 0.85e-9$ # H
- $Ls = 0.25e-9$ # H


If Ls and Lg value sweeps, only $Gm1$, $Re\{Zin\}$, $Im\{Zin\}$, and $|S11|$ plots behavior should change because these plots are depend on the value used for Lg and Ls in addition to Part A parameters.

C


Coupled-tank load (transformer)

- $L11 = 1.9e-9$
- $L12 = 1.6e-9$
- $C11 = 0.5e-12$
- $C12 = 0.5e-12$
- $k = 0.55$
- $Q1 = 8.2$
- $Q2 = 2.0$


|Gm1| vs Frequency (uses per-case Lg/Ls/gm2)

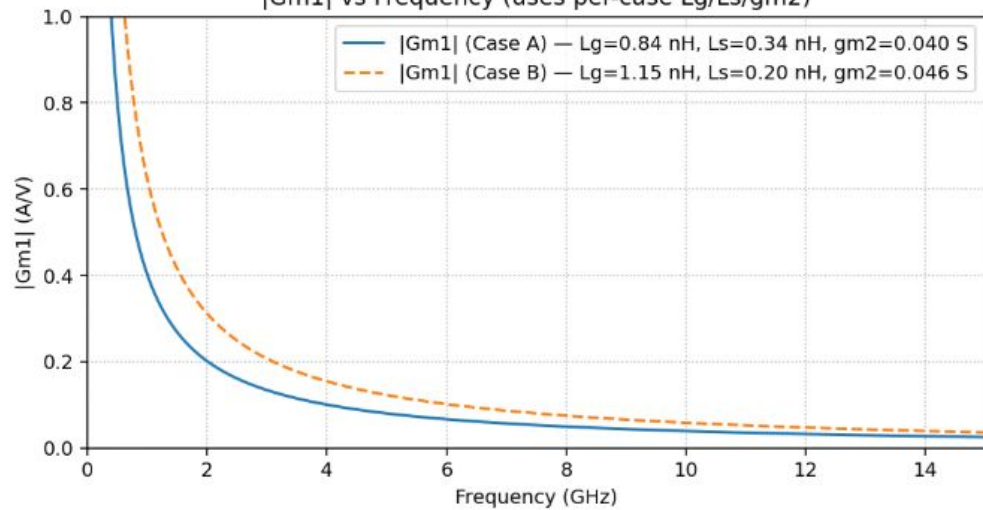


Phase of Gm1 (Eq. 3)

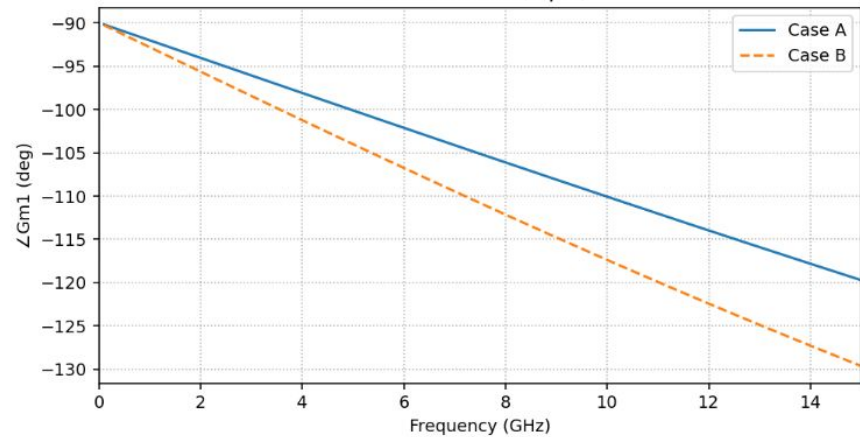

Case A ($L_D=1$ nH, $C_D=2.5$ pF, $L_g=0.85$ nH, $L_s=0.25$ nH, $gm_2=0.10$): Z_{in} & $|S_{11}|$ — ideal vs series-Resistance vs parallel- R_p

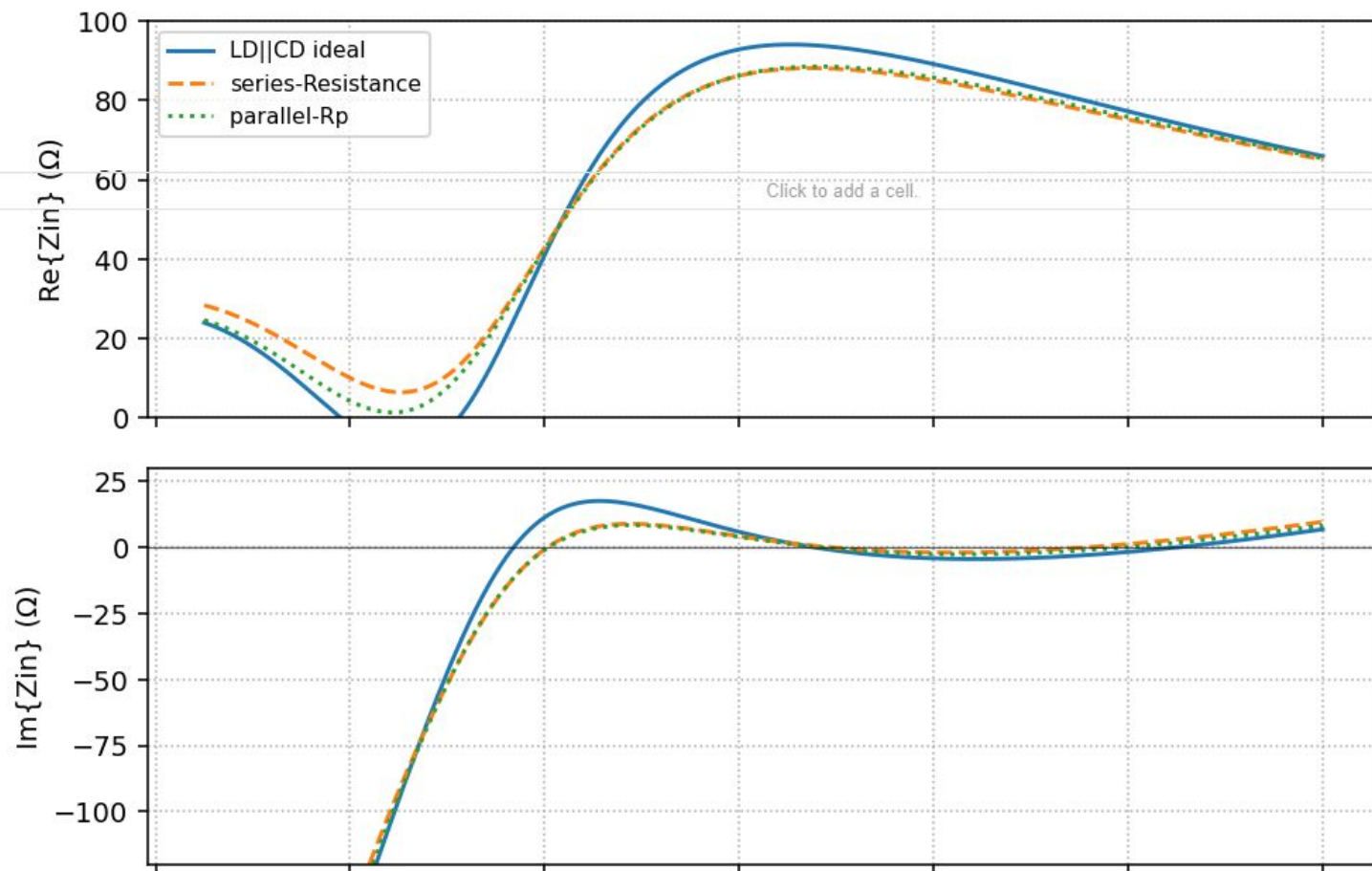

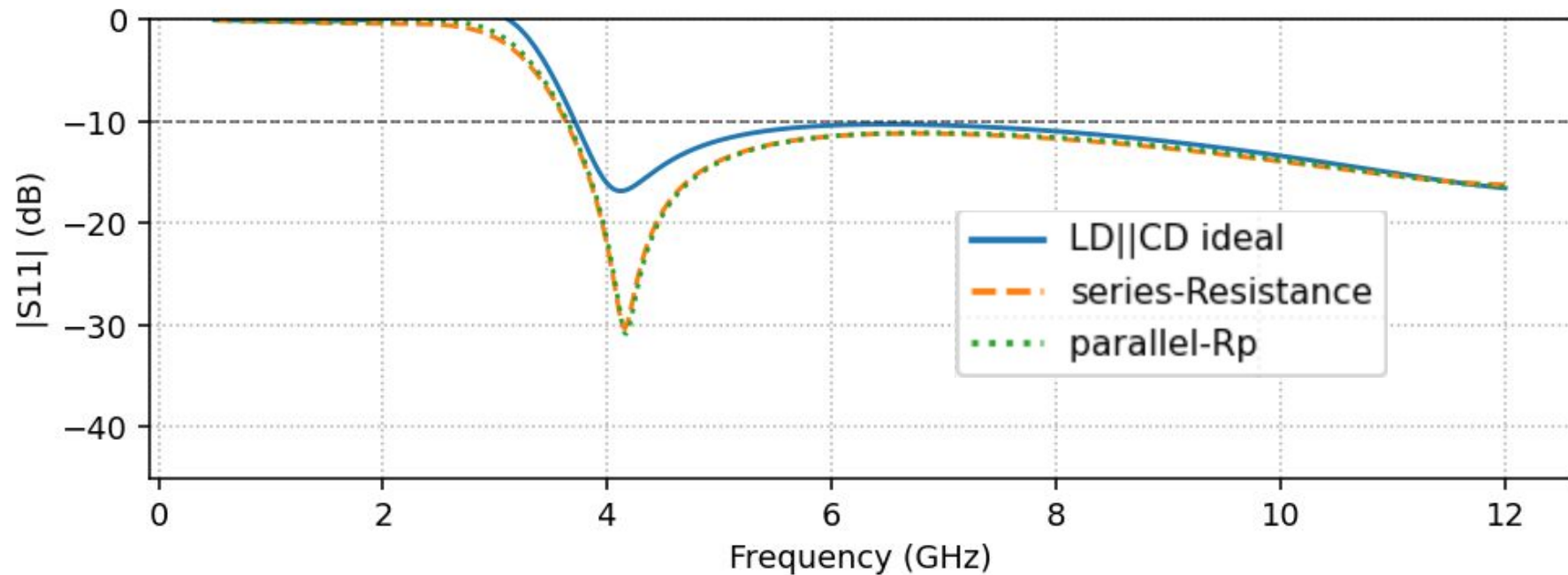

$|S_{11}| \leq -10$ dB

$L_g=0.84\text{nH}$, $L_s=0.25\text{nH}$ \rightarrow exact
with papers table II values

how the curves move what to tweak, and why

Why the real part $\Re\{Z_{in}\}$ sits on a plateau

Starting from Eq. (5) with the paper's intuition limits (set $C_{gd1} \rightarrow 0$, $G_{ds1} \rightarrow 0$ just to expose the dominant term),

$$Z_{in} = \frac{1+T}{j\omega C_{gs1}}, \quad T = j\omega L_S (g_{m1} + j\omega C_{gs1} + G_{ds1}),$$

which gives

$$Z_{in} = \underbrace{\frac{1}{j\omega C_{gs1}}}_{\text{imag}} + \underbrace{\frac{g_{m1} L_S}{C_{gs1}}}_{\text{real, flat plateau}} + \underbrace{j\omega L_S}_{\text{imag}}.$$

Hence the main *lifter*

$$\Re\{Z_{in}\} \approx \frac{g_{m1} L_S}{C_{gs1}}.$$

What moves what (plateau height).

- $\uparrow L_S \Rightarrow \uparrow$ plateau (higher $\Re\{Z_{in}\}$).
- $\uparrow g_{m1} \Rightarrow \uparrow$ plateau; $\uparrow C_{gs1} \Rightarrow \downarrow$ plateau.
- Finite G_{ds1} and any real part seen through the drain path (via C_{gd1}) also add positive real part, helping to keep $\Re\{Z_{in}\} > 0$.

Drain path seen through C_{gd1}

Using Eq. (6) with the paper's stated limits $g_{m2} \gg \omega C_{gs2}$ and $\omega^2 L_P C_{gs2} \ll 1$,

$$Z_D \approx \frac{1}{g_{m2}} + \frac{j\omega L_D}{1 - \omega^2 L_D C_D}.$$

This Z_D couples to the input through C_{gd1} , contributing:

- an *effective capacitance* $C_D^{\text{eff}}(\omega)$ that grows with frequency (from the L_D – C_D tank),
- a *real* term (notably $1/g_{m2}$, and any tank loss such as finite Q or a parallel R_p), which further lifts $\Re\{Z_{in}\}$ and broadens/shallows the match.

What sets the Dip frequency and how low it goes

From S_Parameters

$$S_{11} = \frac{Z_{in} - 50}{Z_{in} + 50}, \quad Z_{in} = R + jX \quad |S_{11}| = \frac{\sqrt{(R - 50)^2 + X^2}}{\sqrt{(R + 50)^2 + X^2}}, \quad R = \Re\{Z_{in}\}, X = \Im\{Z_{in}\}$$

Dip frequency in |S₁₁|: where the Im plot crosses 0, or where the reactance is zero $X = \Im\{Z_{in}\} = 0$

$$|S_{11}|_{\text{dip}} = \left| \frac{R - 50}{R + 50} \right|, \quad \text{Depth (dB)} = 20 \log_{10} \left| \frac{R - 50}{R + 50} \right|$$

At Zero-crossing $X = 0$, the formula reduced to

SO, the closer $R = \Re\{Z_{in}\}$ is to 50Ω at that same frequency, the deeper the dip

- If $R = 50 \Omega \rightarrow$ ideal match $\rightarrow |S_{11}| = 0$ ($-\infty$ dB).
- If $R = 60 \Omega \rightarrow$ depth $\approx 20 \log_{10}(10/110) \approx -20.8$ dB.
- If $R = 40 \Omega \rightarrow$ depth $\approx 20 \log_{10}(10/90) \approx -19.1$ dB.

$$Z_D(s) = \frac{1}{g_{m2}} + Z_{\text{tank}}(s) \quad Z_{\text{tank}}(s) = \frac{sL_D}{1 + \frac{sL_D}{R_p} + s^2L_DC_D}$$

Tank Poles

Parallel Rp||LD||CD that sits inside ZD:

For a parallel RLC the characteristic equation is

$$s^2 + \frac{1}{R_p C_D} s + \frac{1}{L_D C_D} = 0$$

$$s_p = -\frac{1}{2R_p C_D} \pm j \sqrt{\frac{1}{L_D C_D} - \left(\frac{1}{2R_p C_D}\right)^2}$$

From this:

$$\omega_0 = \frac{1}{\sqrt{L_D C_D}}$$

$$Q \approx R_p \sqrt{\frac{C_D}{L_D}} \text{ (for light damping).}$$

$$s_{p1,2} = -2.403846 \times 10^8 \pm j 1.961014 \times 10^{10} \text{ rad/s}$$

Tank Zeros

Its the frequency where $\text{Im}\{Z_{in}\}=0$

$$f_{\text{dip}} \approx \frac{1}{2\pi\sqrt{L_G C_{\text{eff}}}}, \quad C_{\text{eff}} \approx C_{gs1} + C_D^{\text{eff}}(\omega) \text{ (seen through } C_{gd1})$$

Knobs : $\uparrow \text{LGL}$ or $\uparrow \text{CD} \rightarrow$ dip left or $\downarrow \text{CD} \rightarrow$ dip right

$$s_{z1,2} = \frac{-L_D \left(g_{m2} + \frac{1}{R_p} \right) \pm \sqrt{\left[L_D \left(g_{m2} + \frac{1}{R_p} \right) \right]^2 - 4L_D C_D}}{2L_D C_D}$$

$$s_{z1,2} = -7.932692 \times 10^9 \pm j 1.793566 \times 10^{10} \text{ rad/s}$$

The poles and zeros above is just for LD=1nH. For LD=100nH can be managed to get using the formulas above. Main thing to note is that if we change variables of the Tank, we don't get the same poles and zeros. Therefore, use the formula.

Why $|S_{11}| \leq -10$ dB Return Loss Matters

Return loss (RL) is $\rightarrow 20 \cdot \log_{10} |\Gamma|$

For $RL = -10$ dB $\Rightarrow |\Gamma| = 10^{(-10/20)} \approx 0.316$


$VSWR = (1 + |\Gamma|) / (1 - |\Gamma|) \Rightarrow VSWR \approx 1.92$.

Power reflection coefficient = $|\Gamma|^2 \approx 0.10 \Rightarrow$ about 10% reflected, 90% accepted.

Mismatch loss = $-10 \cdot \log_{10}(1 - |\Gamma|^2) \approx 0.46$ dB.

Derivation of 2nd & 3rd stage gain

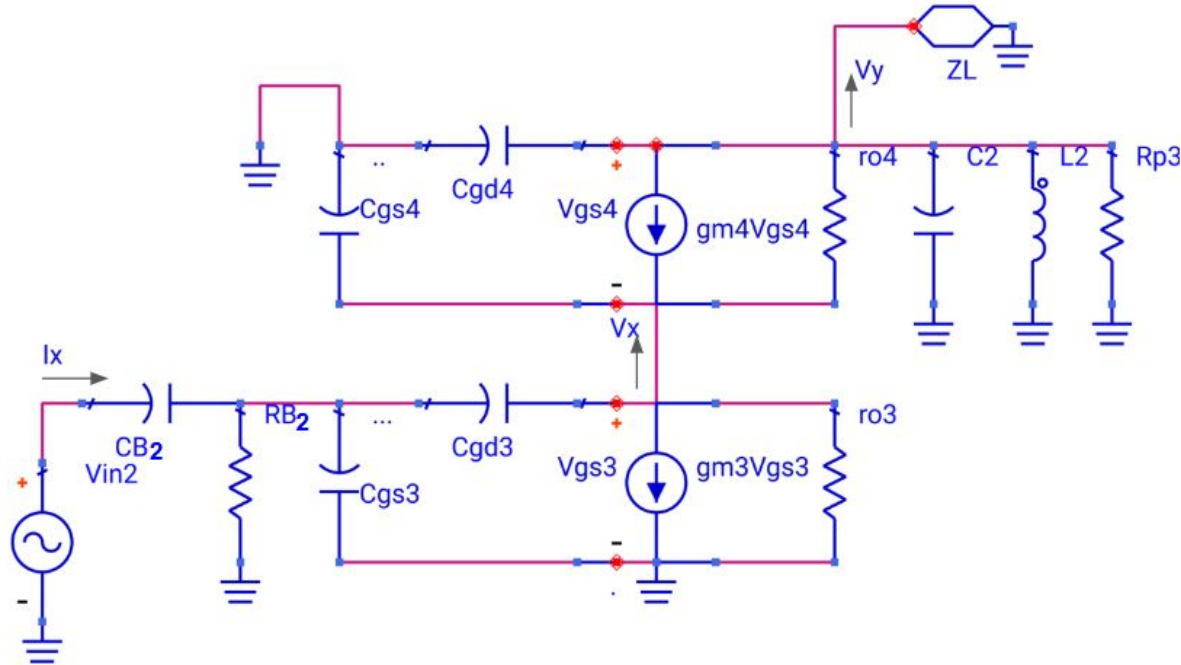Small signal Model for 2nd and 3rd stage Gain analysis



→ 2nd & 3rd stage small signal are exactly similar. Just only number different such as instead of $L_2, C_2, g_{m3}V_{gs3}$ & 4, R_{p3} , use $L_4, L_4, g_{m5}V_{gs5}$ & 6, R_{p4} . for the rest refer the papers schematics Fig.2 (a)

Gain Derivation (M3-M4, M5-M6) with CB2,CB3 and RB1,RB2

Model & Definitions

Used the midband Razavi small-signal model:

- **M3 and M5 (CS)**: controlled source gm_3v_{gs3}, gm_5v_{gs5} from drain to source and ro_3, ro_5 from drain to source, source is AC ground, so $v_{gs3}=v_{g3}, v_{gs5}=v_{g5}$.
- **M4 and M6 (CG cascode)**: gate AC-GND; controlled source gm_4v_{gs4} from drain to source with $v_{gs4}=-V_x, v_{gs6}=-V_x$ (where V_x is M3/M5 drain/M4/M6 source), and ro_4/ro_6 between M4/M6 drain(V_y) and source (V_x).
- **Shunt tanks at the source node V_y** : $L_2||C_2||R_{p3}$ and $L_3||C_3||R_{p4}$. (R_{p1} & R_{p2} used in first stage transformer tank)
- **The input gate high-pass**: formed by C_{b2}/C_{B3} and R_{B1}/R_{B2} .

$$H_{HP2}(s) \triangleq \frac{v_{g3}}{v_{in,2}} = \frac{s R_B C_{B2}}{1 + s R_B C_{B2}}, \quad H_{HP3}(s) \triangleq \frac{v_{g5}}{v_{in,3}} = \frac{s R_B C_{B3}}{1 + s R_B C_{B3}}, \quad s = j\omega.$$

- **Load admittance at V_y** :

$$Y_L(s) = \frac{1}{R_{p3}} + sC_2 + \frac{1}{sL_2}, \quad Y_{L3}(s) = \frac{1}{R_{p4}} + sC_3 + \frac{1}{sL_3}, \quad Z_L(s) = \frac{1}{Y_L(s)}.$$

Gain Derivation (M3-M4) with CB2 and RB

KCL at V_y (output node):

$$(Y_L(s) + \frac{1}{r_{o4}}) v_y + (g_{m4} - \frac{1}{r_{o4}}) v_x = 0.$$

Solve for v_y :

$$v_y = -\frac{g_{m4} - \frac{1}{r_{o4}}}{Y_L(s) + \frac{1}{r_{o4}}} v_x. \quad (1)$$

At V_x (Cascode Source):

$$\left(\frac{1}{r_{o3}} + \frac{1}{r_{o4}} - g_{m4}\right) v_x - \frac{1}{r_{o4}} v_y = g_{m3} v_{g3} \quad (2)$$

Substitute (1) into (2) and solve for v_x/v_{g3} :

$$\left[\frac{1}{r_{o3}} + \frac{1}{r_{o4}} - g_{m4} + \frac{\frac{1}{r_{o4}}(g_{m4} - \frac{1}{r_{o4}})}{Y_L(s) + \frac{1}{r_{o4}}}\right] v_x = g_{m3} v_{g3},$$

$$\Rightarrow \frac{v_x}{v_{g3}} = \frac{g_{m3}}{\frac{1}{r_{o3}} + \frac{1}{r_{o4}} - g_{m4} + \frac{\frac{1}{r_{o4}}(g_{m4} - \frac{1}{r_{o4}})}{Y_L(s) + \frac{1}{r_{o4}}}}$$

Then v_y/v_{g3} follows from (1)

$$\frac{v_y}{v_{g3}} = -\frac{g_{m4} - \frac{1}{r_{o4}}}{Y_L(s) + \frac{1}{r_{o4}}} \frac{v_x}{v_{g3}} \quad (3)$$

Gate-referenced stage gain:

Combine equation (2) and (3)

$$A_{v2, \text{gate}}(s) \equiv \frac{v_y}{v_{g3}} = -g_{m3} \frac{g_{m4} - \frac{1}{r_{o4}}}{\left(\frac{1}{r_{o3}} + \frac{1}{r_{o4}} - g_{m4}\right)\left(Y_L(s) + \frac{1}{r_{o4}}\right) + \frac{1}{r_{o4}}\left(g_{m4} - \frac{1}{r_{o4}}\right)}$$

A useful identity to simplify the denominator is

$$\left(\frac{1}{r_{o3}} + \frac{1}{r_{o4}} - g_{m4}\right)\frac{1}{r_{o4}} + \frac{1}{r_{o4}}\left(g_{m4} - \frac{1}{r_{o4}}\right) = \frac{1}{r_{o3}r_{o4}},$$

so the full denominator equals

$$\left(\frac{1}{r_{o3}} + \frac{1}{r_{o4}} - g_{m4}\right)Y_L(s) + \frac{1}{r_{o3}r_{o4}}.$$

Including the Input high-pass

Since $v_{g3} = H_{\text{HP2}}(s) v_{\text{in},2}$, the input-referenced 2nd-stage gain is

$$A_{v2}(s) \equiv \frac{v_y}{v_{\text{in},2}} = H_{\text{HP2}}(s) A_{v2, \text{gate}}(s) = \frac{sR_B C_{B2}}{1 + sR_B C_{B2}} A_{v2, \text{gate}}(s).$$

Final Gain Expression for 2nd and 3rd stage

The derivation is similar for both stage gain expression:

$$A_{v2}(s) = \underbrace{\frac{s R_B C_{B2}}{1 + s R_B C_{B2}}}_{\text{input HPF}} \left[-g_{m3} \frac{g_{m4} - \frac{1}{r_{o4}}}{\left(\frac{1}{r_{o3}} + \frac{1}{r_{o4}} - g_{m4} \right) \underbrace{\left(\frac{1}{R_{p2}} + s C_2 + \frac{1}{s L_2} + \frac{1}{r_{o4}} \right)}_{Y_{L2}(s)} + \frac{1}{r_{o4}} \left(g_{m4} - \frac{1}{r_{o4}} \right)} \right]$$

Second Stage Gain

$$A_{v3}(s) = \underbrace{\frac{s R_B C_{B3}}{1 + s R_B C_{B3}}}_{\text{input HPF}} \left[-g_{m5} \frac{g_{m6} - \frac{1}{r_{o6}}}{\left(\frac{1}{r_{o5}} + \frac{1}{r_{o6}} - g_{m6} \right) \underbrace{\left(\frac{1}{R_{p4}} + s C_3 + \frac{1}{s L_3} + \frac{1}{r_{o6}} \right)}_{Y_{L3}(s)} + \frac{1}{r_{o6}} \left(g_{m6} - \frac{1}{r_{o6}} \right)} \right]$$

Third stage Gain

Final Gain Expression for 2nd and 3rd stage

The derivation is similar for both stage gain expression:

$$Z_{L2}(s) = \frac{1}{\frac{1}{R_{p3}} + sC_2 + \frac{1}{sL_2}}, \quad Z_{L3}(s) = \frac{1}{\frac{1}{R_{p4}} + sC_3 + \frac{1}{sL_3}}$$

$$H_{HP2}(s) = \frac{sR_B C_{B2}}{1 + sR_B C_{B2}}, \quad H_{HP3}(s) = \frac{sR_B C_{B3}}{1 + sR_B C_{B3}}$$

Voltage divider in the s-domain

$$\frac{v_{g3}}{v_{in,2}} = \frac{Z_R}{Z_R + Z_C} = \frac{R_B}{R_B + \frac{1}{sC_{B2}}} = \frac{sR_B C_{B2}}{1 + sR_B C_{B2}}$$


$$r_{o,cas2} = \frac{1}{g_{ds3}} + \frac{1}{g_{ds4}} + \frac{g_{m4}}{g_{ds3}g_{ds4}}$$

$$r_{o,cas3} = \frac{1}{g_{ds5}} + \frac{1}{g_{ds6}} + \frac{g_{m6}}{g_{ds5}g_{ds6}}$$

$$A_{v2}(s) = H_{HP2}(s) \left[-g_{m3} (Z_{L2}(s) \parallel r_{o,cas2}) \right]$$

$$A_{v3}(s) = H_{HP3}(s) \left[-g_{m5} (Z_{L3}(s) \parallel r_{o,cas3}) \right]$$

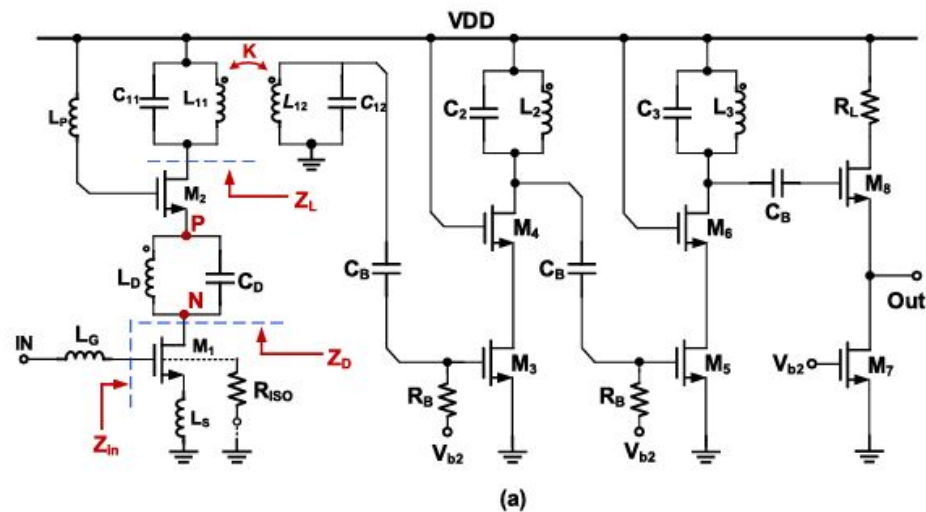Compacted Second and Third stage
Gain expression



A Cryogenic Broadband Sub-1-dB NF CMOS Low Noise Amplifier for Quantum Applications

Razavi's Cascode CS stage with Inductive Degeneration

$$R_X = \frac{R_1 + r_{O2}}{1 + g_m r_{O2}}, \quad \text{Eqn(5.99)} \quad \frac{V_X}{V_G} = \frac{R_S}{L_1 \omega_0} \cdot \frac{R_1 + r_{O2}}{(1 + g_{m2} r_{O2})(R_S + L_G \omega_0)}.$$

- Razavi's $R_X \rightarrow$ "Resistance seen looking up from node x into $M_2 + \text{tank}$ "
- Ours $r_{o,cas2} \rightarrow$ "Resistance seen looking up from the drain of M_3 into $M_4 + r_{o,s}$ (and similarly for stage 3)"
- Eqn 5.99 of Razavi's is playing same role as the effective load $(Z_L(j\omega_0) \parallel r_{o,cas})$
- Eqn 5.100 Razavi's gain $A_v = \frac{V_X}{V_G} \cdot \frac{V_{out}}{V_X}$

equivalent to my notations $A_v = H_{HP}(s) \cdot [-g_m(Z_L \parallel r_{o,cas})]$

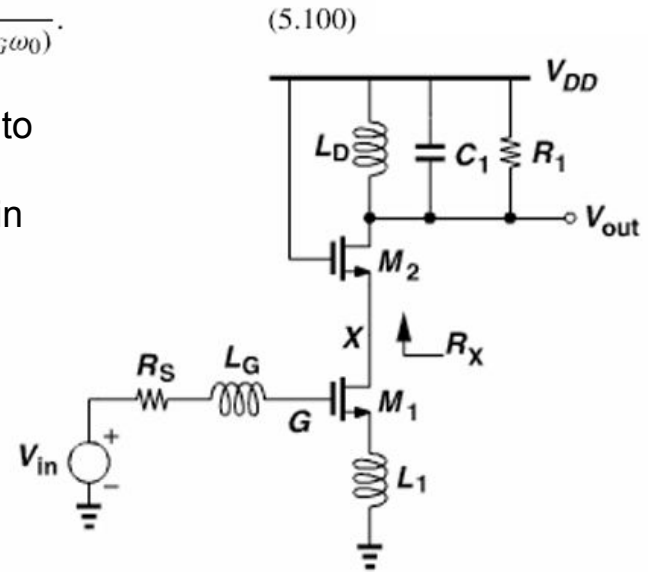


Figure 5.37 Inductively-degenerated cascode CS LNA.

Equivalent relation at resonant

$$R_X \longleftrightarrow (Z_{L2} \parallel r_{o,cas2}), \quad g_{m2} \longleftrightarrow g_{m4}, \quad R_1 \longleftrightarrow R_{p3},$$

Final Gain expression from Razavi

$$A_v \triangleq \frac{V_{out}}{V_{in}} = \frac{\omega_T R_1}{2 \omega_0 R_S} = \frac{R_1}{2 L_1 \omega_0}$$

The first term

$$A_v = \frac{\omega_T R_1}{2 \omega_0 R_S} \quad (5.97)$$

Transconductance x load resistance

$$A_v = \frac{R_1}{2 L_1 \omega_0} \quad (5.98)$$

Note

My gain expressions are longer because I keep the full s-domain transfer (tank frequency response, RC high-pass, finite cascode r_o , and tank R_p). Razavi's final formula for Fig. 5.37 is the special case at resonance under matching assumptions, which reduces our result to $A_v \approx -g_m R_p$ and then further to $\omega_T R_1 / (2 \omega_0 R_S)$

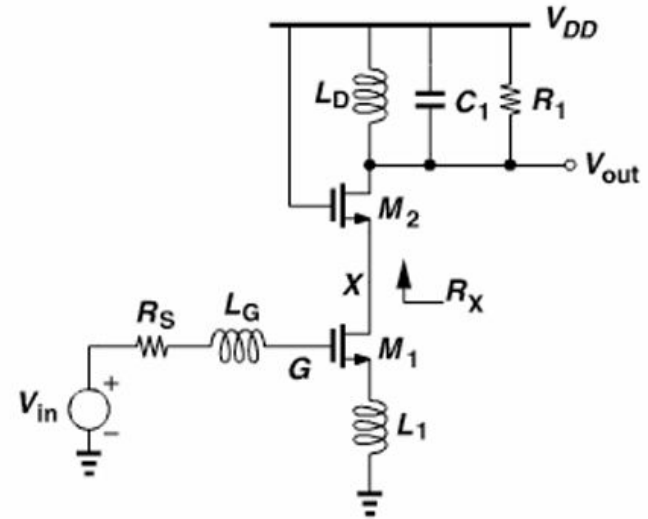


Figure 5.37 Inductively-degenerated cascode CS LNA.

To show how my long expression collapses to Razavi's one

- If I impose the same assumptions Razavi uses, my formula shrinks:

1. Evaluate at resonance:

$$s = j\omega_{02}, \text{ so } Z_{L2}(j\omega_{02}) \approx R_{p3}$$

2. If the cascode is strong:

$$r_{o,\text{cas2}} \gg R_{p3}, \text{ then } Z_{L2} \parallel r_{o,\text{cas2}} \approx R_{p3}$$

3. If the high-pass $\ll \omega_{02}$

$$|H_{\text{HP2}}(j\omega_{02})| \approx 1$$

Then the final expression becomes to

$$A_{v2,\text{max}} \approx -g_{m3}R_{p3}$$

He then rewrites g_m and R_1 in terms of ω_T , ω_0 , R_S , L_1 to get that very compact $\frac{\omega_T R_1}{2\omega_0 R_S}$

Razavi's CS with Inductive Load gain Formulas

Fig. 5.11, Eq. 5.3.1

$$Z_T = \frac{L_1 s + R_S}{L_1 C_1 s^2 + R_S C_1 s + 1}, \quad (5.30)$$

and the tank voltage by $(I_X - g_m V_X)Z_T$. Adding the voltage drop across C_F to the tank voltage, we have

$$V_X = \frac{I_X}{C_F s} + (I_X - g_m V_X)Z_T. \quad (5.31)$$

Substitution of Z_T from (5.30) gives

$$Z_{in}(s) = \frac{V_X}{I_X} = \frac{L_1(C_1 + C_F)s^2 + R_S(C_1 + C_F)s + 1}{[L_1 C_1 s^2 + (R_S C_1 + g_m L_1)s + 1 + g_m R_S]C_F s}. \quad (5.32)$$

This is the same parallel-RLC load expression used in my stages:

$$Z_{L2}(s) = \left(\frac{1}{R_{p3}} + sC_2 + \frac{1}{sL_2} \right)^{-1}, \quad Z_{L3}(s) = \left(\frac{1}{R_{p4}} + sC_3 + \frac{1}{sL_3} \right)^{-1}$$

$$\frac{Y(s)}{Q(s)} = \frac{1}{1 + H(s)}. \quad (12.15)$$

Proper choice of $H(s)$ can yield a *high-pass* response; for example, if $H(s)$ is an ideal integrator [Fig. 12.13(b)],

$$\frac{Y(s)}{Q(s)} = \frac{s}{1 + s}. \quad (12.16)$$

"The gate of M3/M5 is AC-coupled through $C_{B2}(C_{B3})$ and biased by $R_{B2}(R_{B3})$, forming a standard first-order RC high-pass:

$$H_{\text{HP}}(s) = \frac{sR_B C_B}{1 + sR_B C_B}.$$

This has the same single-pole high-pass form as Razavi's $\frac{Y(s)}{Q(s)} = \frac{s}{1+s}$ in *Design of CMOS Phase-Locked Loops* (Eq. 12.16), but here it is implemented with an explicit R_B - C_B coupling network."

$$H_{\text{HP}}(s) = \frac{sR_B C_B}{1 + sR_B C_B}.$$

define a normalized variable

$$\tilde{s} = sR_B C_B,$$

$$H_{\text{HP}}(s) = \frac{\tilde{s}}{1 + \tilde{s}},$$

Zeros and poles for 2nd and 3rd stage

The derivation is similar for both stage gain expression:

Zeros

1. From the tank: as $s \rightarrow 0$, $Y_L(s) \rightarrow \infty$ due to $\frac{1}{sL_2}$, $\frac{1}{sL_3}$ so $A_{v2,v3,\text{gate}}(s) \rightarrow 0$ linearly in s .
 $\Rightarrow s = 0$ is a zero of $A_{v2,v3,\text{gate}}(s)$
2. From the input high-pass: $H_{\text{HP}}(s)$ contributes a zero at $s = 0$.
 $\Rightarrow s = 0$ is a second (coincident) zero of $A_{v2,v3}(s)$.

Thus, the *input-referenced* stage has a double zero at the origin:

zeros: $z_1 = 0$, $z_2 = 0$.

Zeros and poles for 2nd and 3rd stage

The derivation is similar for both stage gain expression:

Poles for A_{v2} :Tank pair are the roots of;

$$(g_{ds3} + g_{ds4} - g_{m4}) C_2 s^2 + \left[(g_{ds3} + g_{ds4} - g_{m4}) \frac{1}{R_{p2}} + g_{ds3} g_{ds4} \right] s + (g_{ds3} + g_{ds4} - g_{m4}) \frac{1}{L_2} = 0,$$

With,

$$s_{p1,2} = \frac{- \left[(g_{ds3} + g_{ds4} - g_{m4}) \frac{1}{R_{p2}} + g_{ds3} g_{ds4} \right] \pm \sqrt{\left((g_{ds3} + g_{ds4} - g_{m4}) \frac{1}{R_{p2}} + g_{ds3} g_{ds4} \right)^2 - 4 (g_{ds3} + g_{ds4} - g_{m4})^2 \frac{C_2}{L_2}}}{2 (g_{ds3} + g_{ds4} - g_{m4}) C_2}.$$

HPF adds one real pole at $p_0 = -1/(R_B C_{B2})$

Zeros and poles for 2nd and 3rd stage

The derivation is similar for both stage gain expression:

Poles for A_{v3} :Tank pair are the roots of;


$$(g_{ds5} + g_{ds6} - g_{m6}) C_3 s^2 + \left[(g_{ds5} + g_{ds6} - g_{m6}) \frac{1}{R_{p4}} + g_{ds5} g_{ds6} \right] s + (g_{ds5} + g_{ds6} - g_{m6}) \frac{1}{L_3} = 0,$$

With,

$$s_{q1,2} = \frac{- \left[(g_{ds5} + g_{ds6} - g_{m6}) \frac{1}{R_{p4}} + g_{ds5} g_{ds6} \right] \pm \sqrt{\left((g_{ds5} + g_{ds6} - g_{m6}) \frac{1}{R_{p4}} + g_{ds5} g_{ds6} \right)^2 - 4 (g_{ds5} + g_{ds6} - g_{m6})^2 \frac{C_3}{L_3}}}{2 (g_{ds5} + g_{ds6} - g_{m6}) C_3}$$

HPF adds one real pole at $p_0 = -1/(R_B C_{B3})$

Gain Plots

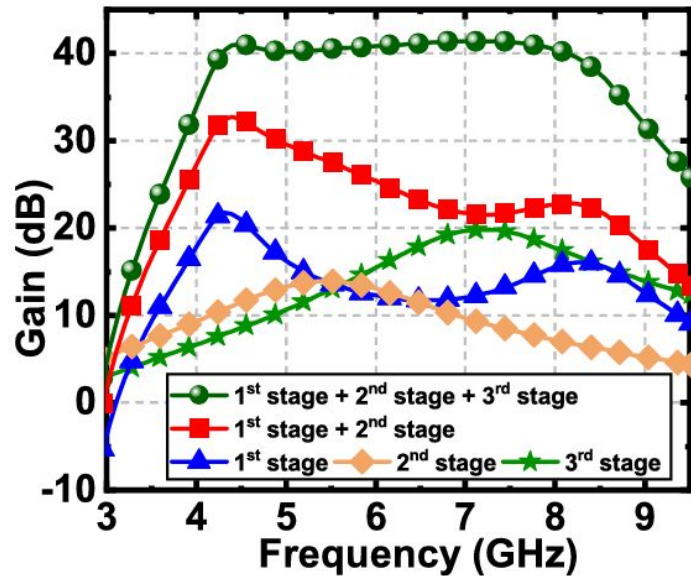


From the paper

(b)

$$Q = \frac{R_p}{\omega_0 L} = \omega_0 C R_p$$
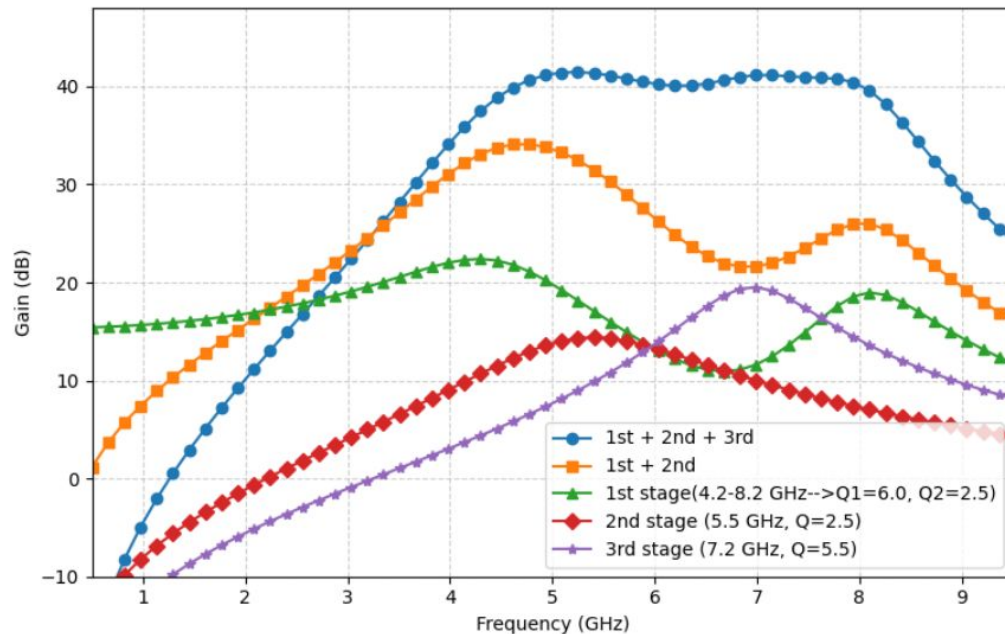
$$R_p = Q \omega_0 L, \quad C = \frac{1}{\omega_0^2 L}$$



Reproducing work

$$R_{p1} \approx 370 \, \Omega, \quad R_{p2} \approx 198 \, \Omega, \quad R_{p3} \approx 86 \, \Omega, \quad R_{p4} \approx 249 \, \Omega.$$

$$\omega_0 = 2\pi f_0,$$

$$C = \frac{1}{\omega_0^2 L},$$

$$R_p = \frac{Q_p}{\omega_0 C} = Q_p \omega_0 L.$$

Stage-2 target:

$$f_{0,2} = 5.50 \text{ GHz}, Q_{p2} \approx 5.0, L_2 = 1.00 \text{ nH}.$$

$$\omega_{0,2} = 2\pi \cdot 5.50 \times 10^9 / \text{s} \approx 3.46 \times 10^{10} / \text{s},$$

$$C_2 = \frac{1}{\omega_{0,2}^2 L_2} \approx \frac{1}{(3.4558 \times 10^{10})^2 \cdot 1.0 \times 10^{-9}} \approx 0.837 \text{ pF},$$

$$R_{p2} = Q_{p2} \omega_{0,2} L_2 \approx 5.0 \cdot (3.4558 \times 10^{10}) \cdot 1.0 \times 10^{-9} \approx 173 \Omega.$$

$$\text{Stage-3 target: } f_{0,3} = 7.20 \text{ GHz}, Q_{p3} = 8.2, L_3 = 1.00 \text{ nH}.$$

$$\omega_{0,3} = 2\pi \cdot 7.20 \times 10^9 / \text{s} \approx 4.52 \times 10^{10} / \text{s},$$

$$C_3 = \frac{1}{\omega_{0,3}^2 L_3} \approx \frac{1}{(4.5239 \times 10^{10})^2 \cdot 1.0 \times 10^{-9}} \approx 0.489 \text{ pF},$$

$$R_{p3} = Q_{p3} \omega_{0,3} L_3 \approx 8.2 \cdot (4.5239 \times 10^{10}) \cdot 1.0 \times 10^{-9} \approx 371 \Omega.$$

Pick gm from a peak-gain target

$$A_{v\text{pk}} \approx g_m R_p \implies g_m \approx \frac{A_{v\text{pk}}}{R_p} \quad (\text{with } A_{v\text{pk}} \text{ in linear, not dB})$$

Stage-2: target peak $\approx 15.0 \text{ dB}$,

$$A_{v\text{pk}} = 10^{15/20} \approx 5.623 \implies g_{m3} \approx \frac{5.623}{173} \approx 0.0330 \text{ S}.$$

Stage-3: choose g_{m5} strong but not overpowering,

$$g_{m5} = 0.0700 \text{ S} \implies A_{v\text{pk}} \approx g_{m5} R_{p3} \approx 0.07 \times 371 \approx 26 \quad (\approx 28.3 \text{ dB}).$$

Gate caps from an fT guess

With a simple RF MOS estimate,

$$C_{\text{sum}} \approx \frac{g_m}{2\pi f_T}, \quad C_{gs} \approx 0.8 C_{\text{sum}}, \quad C_{gd} \approx 0.2 C_{\text{sum}}$$

Using $f_T = 100 \text{ GHz}$:

Stage-2 devices (from $g_{m3} \approx 0.0330$ S, $g_{m4} = 0.0900$ S):

$$C_{\text{sum},3} = \frac{0.033}{2\pi \cdot 10^{11}} \approx 52.0 \text{ fF}, \quad C_{gs3} \approx 41.4 \text{ fF}, \quad C_{gd3} \approx 10.4 \text{ fF},$$
$$C_{\text{sum},4} = \frac{0.090}{2\pi \cdot 10^{11}} \approx 143 \text{ fF}, \quad C_{gs4} \approx 115 \text{ fF}, \quad C_{gd4} \approx 28.6 \text{ fF}.$$

Stage-3 devices (from $g_{m5} = 0.0700$ S, $g_{m6} = 0.110$ S):

$$C_{\text{sum},5} = \frac{0.070}{2\pi \cdot 10^{11}} \approx 112 \text{ fF}, \quad C_{gs5} \approx 89.2 \text{ fF}, \quad C_{gd5} \approx 22.3 \text{ fF},$$
$$C_{\text{sum},6} = \frac{0.110}{2\pi \cdot 10^{11}} \approx 175 \text{ fF}, \quad C_{gs6} \approx 140 \text{ fF}, \quad C_{gd6} \approx 35.0 \text{ fF}.$$

Input high-pass corners (series C_B into R_B)

Ignoring the small gate caps for the corner estimate,

$$f_{\text{HP}} \approx \frac{1}{2\pi R_B C_B}.$$

$$\text{Stage-2: } R_{B2} = 50.0 \text{ k}\Omega, \quad C_{B2} = 4.00 \text{ pF} \Rightarrow f_{\text{HP}} \approx \frac{1}{2\pi \cdot 50 \times 10^3 \cdot 4 \times 10^{-12}} \approx 0.800 \text{ MHz}.$$

$$\text{Stage-3: } R_{B3} = 50.0 \text{ k}\Omega, \quad C_{B3} = 1.00 \text{ pF} \Rightarrow f_{\text{HP}} \approx \frac{1}{2\pi \cdot 50 \times 10^3 \cdot 1 \times 10^{-12}} \approx 3.18 \text{ MHz}.$$

Implementation of Noise Analysis of M1

Derivation of Noise Figure

